

## Binary language

(0,1) 2 values

1 - on , 0 - off

← Inc. value  
MSB                    LSB

### First Method of Decimal to Binary

① 2

$$\begin{array}{r} 16 \ 8 \ 4 \ 2 \ 1 \\ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 0 \ 1 \ 0 \end{array}$$

②  $6 = 4 + 2$

$$\begin{array}{r} 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 0 \ 1 \ 1 \ 0 \end{array}$$

③  $25 = 16 + 8 + 1$

$$\begin{array}{r} 16 \ 8 \ 4 \ 2 \ 1 \\ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 1 \ 0 \ 0 \ 1 \end{array}$$

④ 128

$$\begin{array}{r} 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

⑤ 228

$$128 + 64 + 32 + 4$$

$$\begin{array}{r} 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \ 0 \end{array}$$

⑥ 1221

$$1024 + 128 + 64 + 4 + 1$$

$$\begin{array}{r} 1024 \ 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^{10} \ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \end{array}$$

⑦ 1024

$$\begin{array}{r} 1024 \ 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^{10} \ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

## Binary language

(0,1) 2 values

1 - on , 0 - off

$\leftarrow$  Inc. value  
 MSB                    LSB

### First Method of Decimal to Binary

① 2

$$\begin{array}{r} 16 \ 8 \ 4 \ 2 \ 1 \\ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 0 \ 1 \ 0 \end{array}$$

②  $6 = 4 + 2$

$$\begin{array}{r} 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 0 \ 1 \ 1 \ 0 \end{array}$$

③  $25 = 16 + 8 + 1$

$$\begin{array}{r} 16 \ 8 \ 4 \ 2 \ 1 \\ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 1 \ 0 \ 0 \ 1 \end{array}$$

④ 128

$$\begin{array}{r} 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

⑤ 228

$$128 + 64 + 32 + 4$$

$$\begin{array}{r} 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \ 0 \end{array}$$

⑥ 1221

$$1024 + 128 + 64 + 4 + 1$$

$$\begin{array}{r} 1024 \ 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^{10} \ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \end{array}$$

⑦ 1024

$$\begin{array}{r} 1024 \ 512 \ 256 \ 128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ 2^{10} \ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \\ \hline 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

Method  
Second of Decimal to Binary

① 25

2	25	
2	12 - 1	
2	6 - 0	
2	3 - 0	
	1 - 1	

11001

② 256

2	256	
2	128 - 0	
2	64 - 0	
2	32 - 0	
2	16 - 0	
2	8 - 0	
2	4 - 0	
2	2 - 0	
	1 - 0	

100000000

③ 1023

2	1023	
2	511 - 1	
2	255 - 1	
2	127 - 1	
2	63 - 1	
2	31 - 1	
2	15 - 1	
2	7 - 1	
2	3 - 1	
	1 - 1	

1111111111

## Binary to Decimal

$$\textcircled{1} \quad 011010$$

$$16 + 8 + 2 = 26$$

$$\begin{array}{r}
 32 & 16 & 8 & 4 & 2 & 1 \\
 \hline
 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\
 0 & 1 & 1 & 0 & 1 & 0
 \end{array}$$

$$\textcircled{2} \quad 11111101$$

$$128 + 64 + 32 + 16 + 8$$

$$+ 4 + 1 = 253$$

$$\begin{array}{r}
 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\
 \hline
 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\
 1 & 1 & 1 & 1 & 1 & 1 & 0 & 1
 \end{array}$$

Base 2 = Binary

Base 8 = Octal (0 to 7) we take only 3 value, 4, 2, 1.

Base 10 = Decimal

Base 16 = Hexa (0 to 15)

0-9, A B C D E F  
10 11 12 13 14 15

## Octal to Binary

$$\textcircled{1} \quad (6566120)_8 = (?)_2$$

$$\begin{array}{cccccccc}
 4 & 2 & 1 & 4 & 2 & 1 & 4 & 2 & 1 \\
 110 & / & 101 & / & 110 & / & 110 & / & 001 & / & 010 & / & 000 \\
 6 & 5 & 6 & 6 & 1 & 2 & 0
 \end{array}$$

$$\textcircled{2} \quad (06200560)_8 = (?)_2$$

$$\begin{array}{cccccccc}
 4 & 2 & 1 & 4 & 2 & 1 & 4 & 2 & 1 \\
 000 & / & 110 & / & 010 & / & 000 & / & 000 & / & 101 & / & 110 & / & 000 \\
 0 & 6 & 2 & 0 & 0 & 0 & 5 & 6 & 0
 \end{array}$$

Hexadecimal with base 16.

(We take 4 values  $8, 4, 2, 1 \cdot 2^3, 2^2, 2^1, 2^0$ .)

$0-9, 10-A, 11-B, 12-C, 13-D,$   
 $14-E, 15-F$

①  $(ABCDEF19243ED)_{16} \rightarrow \text{binary}$

$\begin{array}{ccccccccccccccccccccc} 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 \\ \underline{0} & \underline{1} & \underline{0} & \underline{1} & \underline{1} & \underline{0} & \underline{0} & \underline{1} & \underline{1} & \underline{0} & \underline{1} & \underline{1} & \underline{1} & \underline{0} & \underline{0} & \underline{0} & \underline{1} & \underline{0} & \underline{0} & \underline{1} & \underline{1} & \underline{1} & \underline{0} & \underline{1} \\ A & B & C & D & F & I & 9 & 2 & 4 & 3 & E & 1 & 0 & 0 & 1 & 1 & 1 & 0 & 0 & 1 & 1 & 1 & 0 & D \end{array}$

②  $5000\ 9\ E8FF5)_{16} \rightarrow (\ )_2$

$\begin{array}{ccccccccccccccccccccc} 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 & 8 & 4 & 2 & 1 \\ \underline{0} & \underline{1} & \underline{0} & \underline{1} & \underline{0} & \underline{0} & \underline{1} & \underline{1} & \underline{1} & \underline{0} & \underline{0} & \underline{0} & \underline{1} & \underline{1} & \underline{1} & \underline{0} \\ 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 9 & E & 8 & F & F & F & 5 \end{array}$

③  $(36556)_8 = (\ )_{16}$

$(\underline{0} \underline{1} \underline{1} \underline{0} \underline{1} \underline{0} \underline{1} \underline{0})_8$

$(\underline{0} \underline{0} \underline{1} \underline{1} \underline{0} \underline{1} \underline{0} \underline{1} \underline{1} \underline{0})_{16}$

3D6E

\* ④  $(1256)_{10} = (\ )_2$

$1024 + 128 + 64$   
 $+ 32 + 8$

$\begin{array}{ccccccccccccccccccccc} 2048 & 1024 & 512 & 256 & 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ \leftarrow & 2^11 & 2^10 & 2^9 & 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ 0 & 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 & 0 & 0 & 1 \end{array}$

$$\textcircled{5} \quad (856)_{10} = (?)_2$$

$$\begin{array}{r} 512 + 258 + 64 \\ + 16 + 8 \\ \hline \end{array}$$

$$\begin{array}{r} 512 \quad 256 \quad 128 \quad 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \quad 1 \\ \underline{-2} \quad \underline{2^8} \quad \underline{2^7} \quad \underline{2^6} \quad \underline{2^5} \quad \underline{2^4} \quad \underline{2^3} \quad \underline{2^2} \quad \underline{2^1} \quad \underline{2^0} \\ 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 0 \end{array}$$

$$\textcircled{6} \quad (10000100\ 1010)_2 = (\ )_{16}$$

$$\begin{array}{r} 8421 \\ \underline{1000} \\ 8 \end{array} \quad \begin{array}{r} 8421 \\ \underline{0100} \\ 4 \end{array} \quad \begin{array}{r} 8421 \\ \underline{1010} \\ 10 \end{array} = 84A$$

$$\textcircled{3} \quad (\text{AFD } 655)_{16} = (+0)_{10}$$

9388608 2047152 524288 131072 32768 8192 2048 512 256 64  
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |  
4194304 1048576 262144 65536 16384 4096 1024 128 32 16 8 4 2 1

$$= (11, 523, 669)_{10}$$

$$\textcircled{8} \quad (1776542)_8 = (\quad)_{10}$$

$$= (523, 617)_{10}$$

$$\textcircled{9} \quad (85\ 94)_{16} = (\quad )_8$$

1000 0101 1001 0100

001 009 019 110 019 100  
(1      0      2      6      2      4)g

$$\textcircled{10} \quad (\text{CAF896})_{16} = (?)_2$$

$$(1010111100010010110)_2$$

$$\textcircled{11} \quad (1221)_8 = (?)_2$$

$$(001010010001)_2$$

$$\textcircled{12} \quad (1AF)_{16} = (?)_2$$

$$(000110101111)_2$$

$$\textcircled{13} \quad (18918)_{16} = (?)_2$$

$$(00011000100100011000)_2$$

$$\textcircled{14} \quad (8F9625)_{16} = (?)_8$$

$$\text{Step 1} \quad (\underbrace{1000}_8 \underbrace{1111}_F \underbrace{1001}_9 \underbrace{0110}_6 \underbrace{0010}_2 \underbrace{0101}_5)_2 =$$

$$\text{Step 2} \quad \begin{array}{cccccccccc} \overline{100} & \overline{011} & \overline{111} & \overline{001} & \overline{011} & \overline{000} & \overline{100} & \overline{101} \\ \overline{4} & \overline{3} & \overline{7} & \overline{1} & \overline{3} & \overline{0} & \overline{4} & \overline{5} \end{array}$$

$$(43713045)_8$$

Hexadecimal conversion to  
octal.

$$\text{Octal :- } \begin{array}{r} 8 \\ \hline 59 \\ - 7 \\ \hline 3 \end{array} \quad (73)_8$$

$$\text{Hexadecimal :- } \begin{array}{r} 16 \\ \hline 59 \\ - 3 \\ \hline 11 \end{array} \quad (3B)_{16}$$

$\Rightarrow 5.8$  into binary

$$(101.110011)_2$$

$$\begin{array}{r}
 0.8 \\
 \times 2 \\
 \hline
 0.6 \\
 \times 2 \\
 \hline
 0.2 \\
 \times 2 \\
 \hline
 0.4 \\
 \times 2 \\
 \hline
 0.8 \\
 \times 2 \\
 \hline
 0.6 \\
 \times 2 \\
 \hline
 0.2
 \end{array}$$

$\Rightarrow 5.7$  into binary

$$(101.10110)_2$$

$\Rightarrow 0.8$

$$(0.1100)_2$$

$$\textcircled{15} \quad (78)_{10} = (?)_{16}$$

$$\begin{array}{ccccccccc}
 128 & 64 & 32 & 16 & 8 & 4 & 2 & & 1 \\
 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\
 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0
 \end{array}$$

$$\begin{array}{r}
 \underline{0100} \quad \underline{1100} \\
 4 \qquad \qquad \qquad 144
 \end{array} \quad (4E)_{16}$$

One's Compliment

$$\begin{array}{r}
 00110 \\
 11001 \\
 \hline
 11111
 \end{array}$$

$$10101$$

$$01010$$

Second Compliment + 1

$$\begin{array}{r} \textcircled{1} & 00000000 \\ \text{1st} & 11111111 \\ \text{2nd} & +1 \\ \hline & 1000000000 \end{array}$$

$$\begin{array}{r} \textcircled{2} & 11111111 \\ \text{1st} & 00000000 \\ \text{2nd} & +1 \\ \hline & 00000001 \end{array}$$

$$\begin{array}{r} \textcircled{3} & 111101111 \\ \text{1st} & 000010000 \\ \text{2nd} & +1 \\ \hline & 000010001 \end{array}$$

$$\begin{array}{r} \textcircled{4} & 000110010 \\ \text{1st} & 111001101 \\ \text{2nd} & +1 \\ \hline & 111001110 \end{array}$$

$$\begin{array}{r} \textcircled{5} & 1001111111 \\ \text{1st} & 0110000000 \\ \text{2nd} & +1 \\ \hline & 0110000001 \end{array}$$

2nd Compliment

$$\begin{array}{r} \textcircled{1} & 1110011100 \\ \text{2nd:} & 0001100100 \end{array}$$

② 00011100000  
2nd: 11100100000

③ 1001010001  
2nd 0110101111

④ 11111110  
2nd 0000010

$(28)_{16}$  into Decimal

1st Method

$\begin{array}{r} 84218421 \\ \underline{00101000} \end{array}$

00101000

32168421 =  $(40)_{10}$

2nd Method  $= 2 \times 16^1 + 8 \times 16^0$   
 $32 + 8$   
 $= 40$

Addition

{  
0+0=0, 0+1=1,  
1+0=1, 1+1=0 carry  
1+1+1=1 carry

① 111001100  
+ 1101110011  
1101111111

② 1010010  
+ 0101110  
10000000

③ 11110000  
+ 10100000  
110010000

④ 110011001  
+ 111111111  
1110011000

$$\begin{array}{r} \overset{2}{\cancel{2}} \overset{2}{\cancel{2}} \overset{2}{\cancel{2}} \\ \times 0000 \\ - 11 \\ \hline 01101 \end{array}$$

5 =

$$\begin{array}{r} \textcircled{5} \quad 10111101010 \\ + 01000010101 \\ \hline \cancel{-100000} \cancel{+110} \\ \hline 11111111111 \end{array}$$

$$\begin{array}{r} \textcircled{6} \quad 100011111 \\ + 100111111 \\ \hline \cancel{+100000} \cancel{11110} \\ \hline 10010 \end{array}$$

$$0-0=0, 1-0=1, 1-1=0$$

$$0-1=1 \text{ with borrow } 1$$

$$\begin{array}{r} \textcircled{7} \quad 1010100 \\ - 0000001 \\ \hline 1010011 \end{array}$$

$$\begin{array}{r} \textcircled{8} \quad \overset{2}{\cancel{1}} \overset{0}{\cancel{1}} \overset{0}{\cancel{1}} 0101 \\ - 010001100 \\ \hline 011101001 \end{array}$$

$$\begin{array}{r} \textcircled{9} \quad 111001001 \\ - 001100010 \\ \hline \cancel{+011000111} \end{array}$$

$$\begin{array}{r} \textcircled{10} \quad 111001100 \\ - 000110111 \\ \hline 110010101 \end{array}$$

⇒ Subtraction with help of 1's compliment.

Carry

$$\begin{array}{r} \textcircled{1} \\ 10 \\ \underline{10} \\ 00 \\ \rightarrow +1 \\ \hline 01 \end{array}$$

No Carry

$$\begin{array}{r} 10 \\ \underline{+00} \\ 10 \\ - (01) \end{array}$$

$$\begin{array}{l} 01 - x \\ 10 - x' \end{array}$$

$$\begin{array}{r} \textcircled{1} \quad \begin{array}{r} x \\ 110010101 \\ 001101010 \end{array} \\ \text{from} \quad \begin{array}{r} y \\ 111110100 \end{array} \end{array}$$

$$\begin{array}{r} \textcircled{1} \\ 111110100 \\ + 001101010 \\ \hline 001011110 \\ + 1 \\ 001011111 - \text{Ans.} \end{array}$$

$$\begin{array}{r}
 \text{(2)} \quad \begin{array}{r} X \\ 110110111 \\ 001001000 \end{array} \quad \text{from} \quad \begin{array}{r} Y \\ 111110101 \end{array} \\
 \begin{array}{r}
 \text{(1)} \\
 111110101 \\
 + 001001000 \\
 \hline
 000111101 \\
 + 1 \\
 \hline
 000111110 - \text{Ans}
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 \text{(3)} \quad \begin{array}{r} X \\ 110110111 \\ 001001000 \end{array} \quad \text{from} \quad \begin{array}{r} Y \\ 11100100 \end{array} \\
 \begin{array}{r}
 \text{(1)} \\
 11100100 \\
 + 00100100 \\
 \hline
 00001000 \\
 + 1 \\
 \hline
 00001001
 \end{array}
 \end{array}$$

Without Carry

$$\begin{array}{r}
 \text{(1)} \quad \begin{array}{r} 110110111 \\ 001001000 \end{array} \quad \text{from} \quad \begin{array}{r} 101110101 \end{array} \\
 \begin{array}{r}
 101110101 \\
 + 001001000 \\
 \hline
 110111101 - \text{Compliment} \\
 -(001000010)
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 \text{(2)} \quad \begin{array}{r} 110110111 \\ 001001000 \end{array} \quad \text{from} \quad \begin{array}{r} 10100100 \end{array} \\
 \begin{array}{r}
 10100100 \\
 + 00100100 \\
 \hline
 11001000 ) \quad 1's \text{ compliment} \\
 -(00110111)
 \end{array}
 \end{array}$$

③ 11001000 from 00011011  
00110111

$$\begin{array}{r} 00011011 \\ + \underline{00110111} \\ \hline 01010010 \\ - (10101101) \end{array}$$

one's  
complement

④ 11010101 from 00010101  
00101010

$$\begin{array}{r} 00010101 \\ + \underline{00101010} \\ \hline 00111111 \\ - (11000000) \end{array}$$

one's  
complement

⑤ 11110011 from 11100110  
00001100

$$\begin{array}{r} 11100110 \\ + \underline{00001100} \\ \hline 11110010 \\ - (00001101) \end{array}$$

one's  
complement

1 Byte = 8 bits

1 Nibble = 4 bits

8 Byte = 64 bits

64 Bits = 16 Nibble

Subtraction with help of 2's complement

①  $\begin{array}{r} 0010100 \\ 2's \text{ C} \quad 1101011 \\ \hline +1 \\ \hline 11010111 \end{array}$  from 10001010

$$\begin{array}{r} 10001010 \\ +11010111 \\ +(01100001) \end{array}$$

② 101000101  
100100010  $\rightarrow$  2's Com. 011011101

$$\begin{array}{r} 101000101 \\ +011011110 \\ +(000100011) \end{array}$$

③ 01011010  
10110101  $\rightarrow$  2's Com. 01001010

$$\begin{array}{r} 10110101 \\ +01001011 \\ \hline 01011010 \end{array}$$

Ans  $(\underline{-01011011})$  2's Compl.

Without carry

① 01001011  
11000101  $\xrightarrow{2's \text{ C}}$  00111010

$$\begin{array}{r} 00111010 \\ +1 \\ \hline 00111011 \end{array}$$

$$\begin{array}{r}
 \text{111111} \\
 01001011 \\
 +00111011 \\
 \hline
 10000110 \rightarrow 2's \\
 -\underline{01111010} \\
 \end{array}$$

$$\begin{array}{r}
 \textcircled{2} \quad 00100101 \\
 -10001010 \rightarrow 2's \\
 \hline
 00100101 \\
 +01110110 \\
 \hline
 10011011 \rightarrow 2's \\
 \underline{01100101} \\
 \end{array}
 \quad \begin{array}{l}
 01110101 \\
 +1 \\
 \hline
 01110110
 \end{array}$$

$$\begin{array}{r}
 \textcircled{3} \quad 1110001 \\
 -0001110 \rightarrow 2's \\
 \hline
 1110001 \\
 +1 \\
 \hline
 1110010
 \end{array}$$

$$\begin{array}{r}
 \textcircled{1} \quad 1110001 \\
 +1110010 \\
 -\underline{(1100011)}
 \end{array}$$

$$\begin{array}{r}
 \textcircled{4} \quad 111111100 \\
 -000111111 \rightarrow 2's \\
 \hline
 111100000 \\
 +1 \\
 \hline
 111100001
 \end{array}$$

$$\begin{array}{r}
 \textcircled{1} \quad 111111100 \\
 +111000001 \\
 -\underline{(11011101)}
 \end{array}$$

$$\begin{array}{r}
 \textcircled{3} \quad \begin{array}{r}
 00010001 \\
 - 11000000
 \end{array} \rightarrow 2's \quad \begin{array}{r}
 \dots\dots \\
 00011111 \\
 + 1 \\
 \hline 00100000
 \end{array} \\
 \begin{array}{r}
 00010001 \\
 + 00100000 \\
 \hline 00110001
 \end{array} \quad \begin{array}{l}
 \text{2's} \\
 \hline 11001111
 \end{array}
 \end{array}$$

## LOGIC GATE

A Device which take decision. A logic Gate is a device which takes acts as a building block for digital circuits. They perform basic logical functions that are fundamental to digital circuits.

## Types of logic gates :-

All the gates are 2 input

- 1. AND
  - 2. OR
  - 3. NOT
  - 4. NOR
  - 5. NAND
  - 6. XOR
  - 7. XNOR
- Basic Gates      Not is one Input Gate
- Inverter, complementor
- Universal Gates       $\Rightarrow D_1$   
 $\Rightarrow D_2$
- Arithmetic Gates

Input is either 0 or 1.

OR GATE  
with respect to c.

$$2^3 = 8$$


x	y	z	output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

e.g.  $(a = b) \text{ OR } (b = c) \text{, OR } (c = d)$

$$2^4 = 16$$

A	B	C	D	output
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1


Symbol of OR GATE (Hardware)

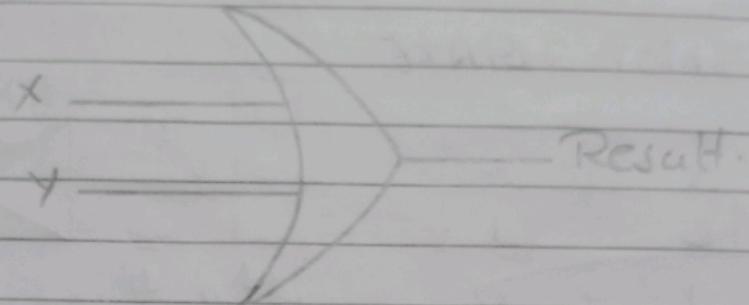

$\Rightarrow$  AND GATE

x	y	r
0	0	0
0	1	0
1	0	0
1	1	1

$$2^3 = 8$$

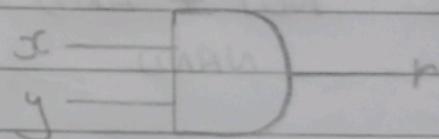

$(+)$  = OR

$(\cdot)$  = AND

	x	y	z	r
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	0
	1	0	0	0
	1	0	1	0
	1	1	0	0
	1	1	1	1

$$\star x + 1 = 1$$

$$x + 0 = x$$

$$x \cdot 1 = x$$


$$x \cdot 0 = 0$$

$$x + x = x$$

$$x \cdot x = x$$

$\Rightarrow$  NOT GATE

x	r
0	1
1	0

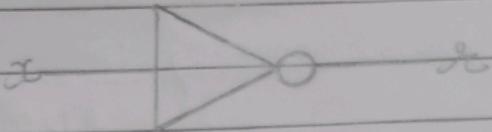


At a time, there is  
only 1 Input.

NOT GATE -  $\bar{x}$

$$2^3 = 8$$

Q1.  
NOT + AND  
NAND

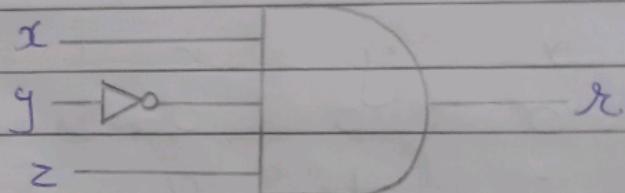

x	y	$\bar{y}$	z	r
0	0	1	0	0
0	1	0	1	0
1	0	1	0	0
1	1	0	1	1
1	0	1	0	0
0	1	0	0	0
0	0	1	1	1

$$2^2 = 4$$

Q2.


$x$	$\bar{x}$	$y$	$\bar{y}$	$r$
0	1	0	1	1
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0




Q3.

$x$	$\bar{x}$	$y$	$\bar{y}$	$r$
0	1	0	1	1
0	1	1	0	1
1	0	0	1	1
1	0	1	0	0

NOT + OR / AND = NOR

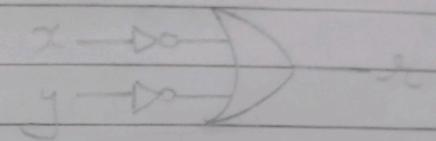


Q4

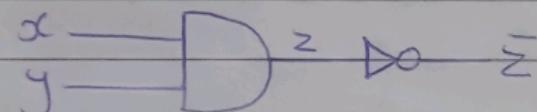

NOT + AND = NAND

$x$	$y$	$z$	$\bar{z}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Q5.

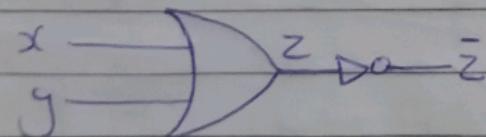

$x$	$y$	$z$	$\bar{z}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


★

$$x + x + x = x$$


$$x + 1 + x = 1$$

$$x + 0 + x = \emptyset x$$

NAND GATE

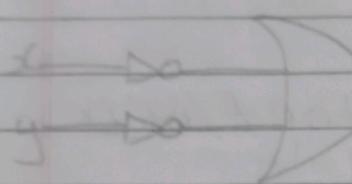

NOR GATE




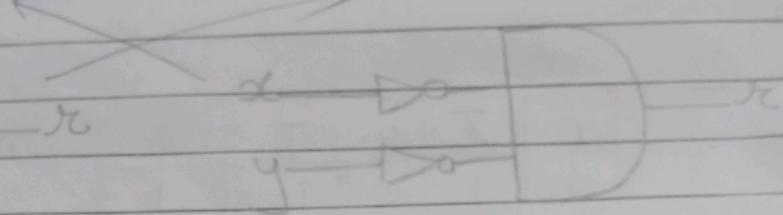


Their symbol as well as result are also different

(I)  $AB + C$

(II)  $(A+B) \cdot C$

(III)  $AB + CD$

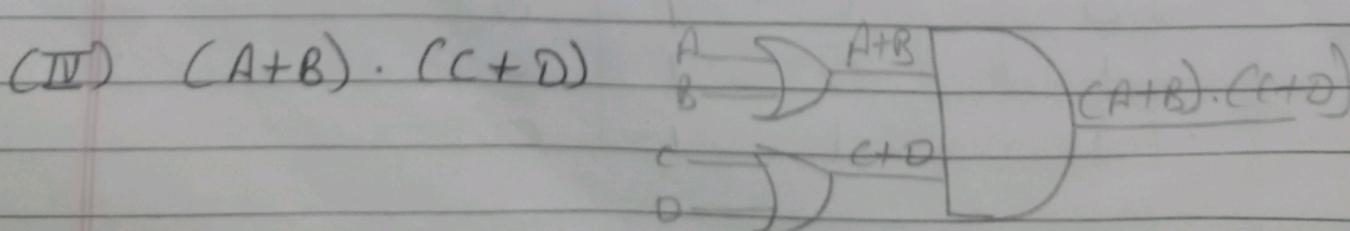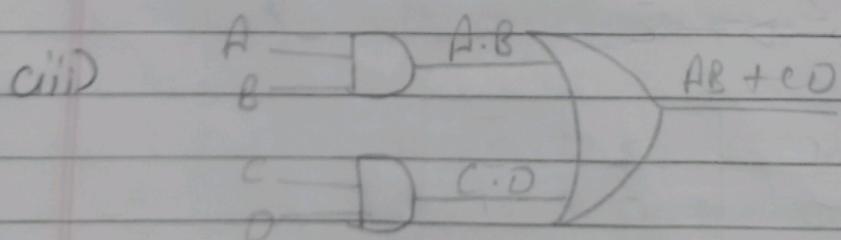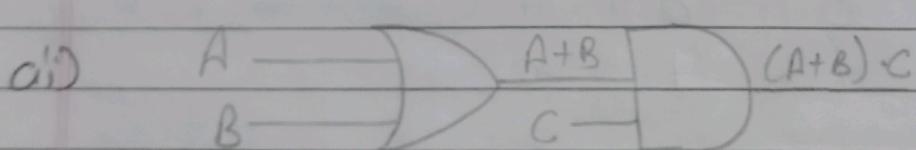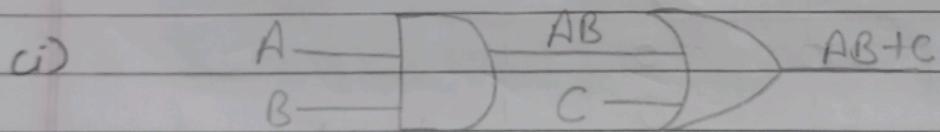

OR = 1 (+)  
AND = 0 (-)

EX-OR

X-OR

Exclusive OR




$$A \oplus B = \bar{A}B + A\bar{B}$$

①  $\bar{A}B + A\bar{B}$

A	B	$\bar{A}$	$\bar{B}$	$\bar{A}B$	$A\bar{B}$	$\bar{A}B + A\bar{B}$
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

If Input is same than result is 0,  
if Input is diff. than result is 1.

Symbol

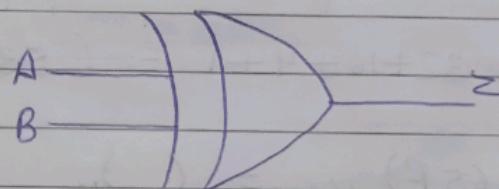

EX-NOR

X-NOR


Exclusive NOR  
( $A \odot B$ )

②  $\bar{A}B + A\bar{B}$

Input		Output				
A	B	AB	$\bar{A}$	$\bar{B}$	$\bar{A}\bar{B}$	$AB + \bar{A}\bar{B}$
0	0	0	1	1	1	1
0	1	0	1	0	0	0
1	0	0	0	1	0	0
1	1	1	0	0	0	1

If Input is same than result is 1. If  
input is diff. than result is 0.

Symbol

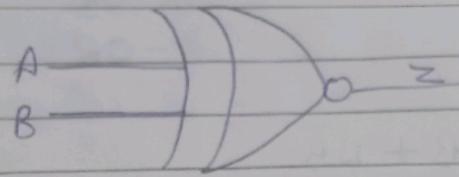

## \* Number System

①  $(110101)_2 = (?)_{10}$

$$\begin{array}{ccccccccc} 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\ & 1 & 1 & 0 & 1 & 0 & 1 \end{array}$$
$$32 + 16 + 4 + 1 = (53)_{10}$$

②  $(B65F)_{16} = (?)_{10}$

$$\begin{array}{cccccccccccccccc} & 16384 & & 4096 & & 1024 & & 256 & & 128 & & 32 & & 64 & & 16 & & 8 & & 4 & & 2 & & 1 \\ 1 & \backslash & 0 & & 1 & \backslash & 1 & \backslash & 0 & & 1 & \backslash & 0 & & 1 & \backslash & 0 & & 1 & \backslash & 1 & & 1 & & 1 \end{array}$$


$$(46687)_{10}$$

③  $(153)_{10} = (?)_8$


$$\begin{array}{cccc} 421 & 421 & 421 \\ 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0 & 1 \\ \hline 2 & 3 & 1 \end{array}$$

$$(231)_8$$
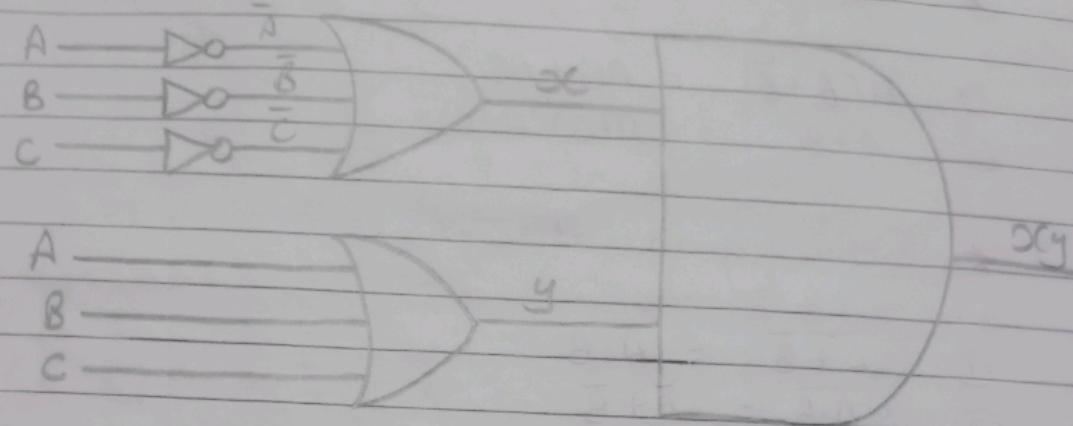
$$\textcircled{3} \quad (\bar{A} + \bar{B} + \bar{C})(A + B + C)$$


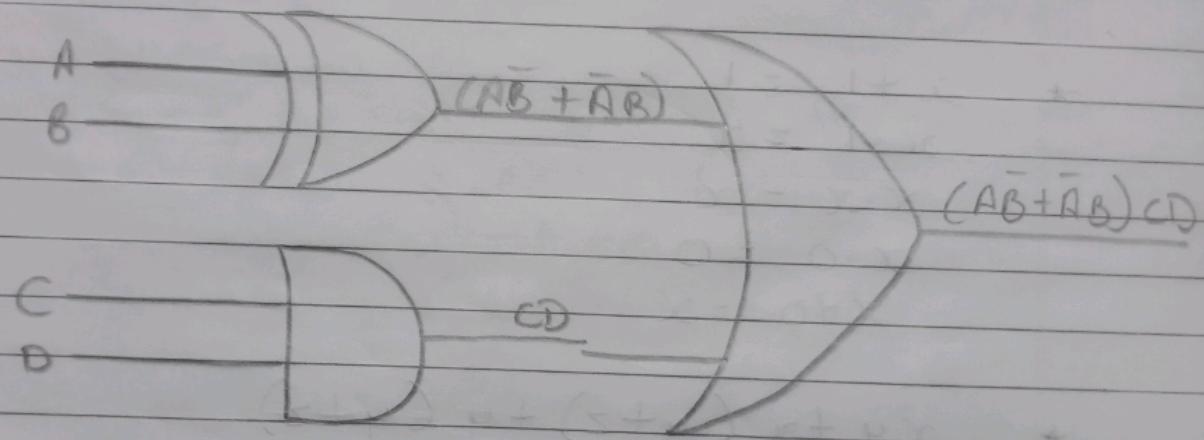
$$\textcircled{4} \quad (AB + \bar{A}\bar{B}) + CD$$



### \* Commutative law

$$\textcircled{1} \quad A+B = B+A$$

$$\textcircled{2} \quad A \cdot B = B \cdot A$$

### \* Associative law

$$\textcircled{1} \quad A + (B+C) = (A+B)+C$$

$$\textcircled{2} \quad A \cdot (BC) = (AB) \cdot (AC) = (AB)C$$

## \* Distributive Law

$$\textcircled{1} \quad A(B+C) = AB+AC$$

$$\textcircled{2} \quad A+BC = (A+B)(A+C)$$

## \* De Morgan's Theorem

$$\textcircled{1} \quad \overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\textcircled{2} \quad \overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\textcircled{3} \quad \overline{A+B+C+D} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$$

$$\textcircled{4} \quad \overline{A \cdot B \cdot C \cdot D} = \bar{A} + \bar{B} + \bar{C} + \bar{D}$$

$$★ \quad x+1 = 1$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot 0 = 0$$

$$x+0 = x$$

$$★ \quad xy + x(y+z) + y(y+z)$$

$$\begin{aligned} & xy + xy + xz + y \cdot y + yz \\ & xy + xz + y + yz \\ & xy + xz + y(1+z) \\ & \quad \quad \quad \underbrace{xy}_{xz} + \underbrace{xz}_{y(x+1)} + y \\ & xz + y \end{aligned}$$

$$★ \quad x(\bar{x}+z)(\bar{x}y+\bar{z})$$

$$(x\bar{x}+xz)(\bar{x}y+\bar{z})$$

$$\left[ \cancel{xx\bar{x}} \cancel{\bar{x}y} + \cancel{xx\bar{z}} + \cancel{xz\bar{x}} \cancel{y} + \cancel{xz\bar{z}} \right] ,$$

$$\cancel{x(x\cdot y)} +$$

$$(0 + xz)(\bar{y} + \bar{z})$$

$$xz(\bar{y} + \bar{z})$$

$$x\bar{z}\bar{y} + xz\bar{z}$$

$$0+0=0$$

\*  $(A+B)(A+C)$

$$AA + AC + BA + BC$$

$$(A(A+C) + B(A+C))$$

$$I + AC + BA + BC$$

$$A(I+C) + B(I+C)$$

$$A + BA + BC - A(I+B) + BC$$

$$A + BC$$

\*  $A(A+B) = A$  (Absorption Law)

$$AA + AB$$

$$I + AB$$

$$A(I+B)$$

$$A = A$$

\*  $\overline{x+y+z+\bar{z}} = \bar{x} \cdot \bar{y} \cdot \bar{z} \cdot \bar{z}$

$$\bar{x} \cdot \bar{y} \cdot \bar{z} \cdot z = 0 \text{ Ans}$$

\*  $\overline{x \cdot y \cdot \bar{z} \cdot \bar{w}} = \bar{x} + \bar{y} + \bar{z} + \bar{w}$

$$= \bar{x} + \bar{y} + z + w$$

$$a+0 = a$$
$$a \cdot 1 = a$$

Identity law

$$a+a' = 1$$
$$a \cdot a' = 0$$

Complement law

★  $A \cdot A = A$

$$A+A = A$$

$$A = A$$

### Questions

①  $A + (B+C) = ? (A+B)+C$

Take  $A = 1, B = 2, C = 3$

$$1 + (2+3) = (1+2) + 3$$

$$1+(5) = (3)+3$$

$$6 = 6$$

Hence Proved

② As per Associative law? If a logical operation of any two variables is performed first and then the same operation is performed with the remaining variable gives the same result.

$$A + (B+C) = (A+B)+C$$

$$A(BC) = (AB)C$$

③ Write down about Distributive law:-

Distributive law states that the multiplication of two variables and adding the result with a variable will result in the same value as multiplication of addition of the variable with individual variables.

$$A+BC = (A+B)(A+C)$$

$$A(CB+CA) = AB + AC$$

$$\textcircled{4} \quad x \cdot y \cdot \bar{z} \cdot z = \bar{x} + \bar{y} + z + \bar{z}$$

$$\underline{x+y+\bar{z} \cdot \bar{w}} = \bar{x} \cdot \bar{y} \cdot z + w$$

$$\textcircled{5} \quad (A+B)(A+C) = ? \quad A+BC$$

$$(A+B)(A+C) = AA + AC + BA + BC$$

$$= A + AC + AB + BC$$

$$= A(1+C+B) + BC$$

$$(A+B)(A+C) = A+BC$$

$$\textcircled{6} \quad (25 \cdot 20)_{10} \text{ to } (?)_2$$

11001.0011

$$\begin{array}{r} \sqrt{201} \\ 2 \\ \hline 40 \\ 2 \\ \hline 80 \\ 2 \\ \hline 160 \\ 2 \\ \hline 120 \end{array}$$

\textcircled{6} Shortcut for 2's Complement :- A shortcut to manually convert a binary number into its two's complement is to start at the least significant bit (LSB), and copy all the zeros, working from LSB toward the most significant bit until the first 1 is reached; then copy that 1 and flip all the remaining bits.

for e.g.  $00110101)_2$  2's  
 $11001011$

# SOP (Sum of Product) =  $AB + CD$  Minterm  
 POS (Product of sum) =  $(A+B)(C+D)$  Max term

x	y	z	sop minterm	pos maxterm
0	0	0	$\bar{x}\bar{y}\bar{z}$	$x+y+z$
0	0	1	$\bar{x}\bar{y}z$	$x+y+\bar{z}$
0	1	0	$\bar{x}y\bar{z}$	$x+\bar{y}+z$
0	1	1	$\bar{x}yz$	$x+\bar{y}+\bar{z}$
1	0	0	$x\bar{y}\bar{z}$	$\bar{x}+y+z$
1	0	1	$x\bar{y}z$	$\bar{x}+y+\bar{z}$
1	1	0	$xy\bar{z}$	$\bar{x}+\bar{y}+z$
1	1	1	$xyz$	$\bar{x}+\bar{y}+\bar{z}$

#  $2^4 = 16$

x	y	w	z	minterm	maxterm
0	0	0	0	$\bar{x}\bar{y}\bar{w}\bar{z}$	$x+y+w+z$
0	0	0	1	$\bar{x}\bar{y}\bar{w}z$	$x+y+w+\bar{z}$
0	0	1	0	$\bar{x}y\bar{w}\bar{z}$	$x+y+\bar{w}+z$
0	0	1	1	$\bar{x}ywz$	$x+y+\bar{w}+\bar{z}$
0	1	0	0	$\bar{x}ywz$	$\bar{x}y+w+z$
0	1	0	1	$\bar{x}y\bar{w}z$	$x+y+w+\bar{z}$
0	1	1	0	$\bar{x}yw\bar{z}$	$x+y+\bar{w}+\bar{z}$
0	1	1	1	$\bar{x}y\bar{w}\bar{z}$	$x+y+w+\bar{z}$
1	0	0	0	$x\bar{y}\bar{w}\bar{z}$	$\bar{x}+y+w+z$
1	0	0	1	$x\bar{y}\bar{w}z$	$\bar{x}+y+w+\bar{z}$
1	0	1	0	$x\bar{y}w\bar{z}$	$\bar{x}+y+\bar{w}+z$
1	0	1	1	$x\bar{y}wz$	$\bar{x}+y+\bar{w}+\bar{z}$
1	1	0	0	$xy\bar{w}\bar{z}$	$\bar{x}+y+w+\bar{z}$
1	1	0	1	$xy\bar{w}z$	$\bar{x}+y+w+\bar{z}$
1	1	1	0	$xyw\bar{z}$	$\bar{x}+y+\bar{w}+\bar{z}$
1	1	1	1	$xywz$	$\bar{x}+y+\bar{w}+\bar{z}$

# min term =  $\Sigma m$   
 max term =  $\prod M$

$$\text{miny} = ABC + \bar{A}BC + A\bar{B}\bar{C} \quad (\text{SOP})$$

$\begin{matrix} ABC \\ \text{m}_7, \text{m}_3, \text{m}_4 \\ \text{m}_0, \text{m}_4, \text{m}_3 \end{matrix}$

$$\begin{matrix} \text{m}_7 \\ \text{m}_3 \\ \text{m}_4 \\ \text{m}_0 \\ \text{m}_4 \\ \text{m}_3 \end{matrix}$$

$$\text{maxy} = A\bar{B}C + ABC + \bar{A}\bar{B}\bar{C}$$

$\text{M}_2, \text{M}_0, \text{M}_6$

#  $A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + ABC$


**SOP** =  $m_6, m_4, m_2, m_7$

**PDS** =  $M_1, M_3, M_5, M_0$

#	A	B	C	R	
0	0	0	0	1	- min
0	0	0	1	1	
0	1	0	0	0	- max
0	1	1	1	0	
1	0	0	0	1	
1	0	1	0	0	
1	1	0	0	0	
1	1	1	1	1	

$$\text{min term } (\Sigma m) = ((\bar{A}\bar{B}\bar{C}) + (\bar{A}\bar{B}C) + (A\bar{B}\bar{C}) + (ABC))$$
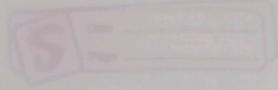
$$\text{max term } (\prod M) = ((A\bar{B}C) + (A\bar{B}\bar{C}) + (\bar{A}\bar{B}\bar{C}) + (\bar{A}\bar{B}C))$$



$$\# \Sigma_m = \bar{A}\bar{B}C + A\bar{B}C + \bar{A}\bar{B}\bar{C}$$

$m_1, m_5, m_2$

$$\Pi M = M_6, M_2, M_5$$

#	A	B	C	result	$\Sigma_m$	$\Pi M$
	0	0	0	0	F	$A\bar{B}C$
	0	0	1	1	$\bar{A}\bar{B}C$	
	0	1	0	1	$\bar{A}\bar{B}\bar{C}$	
	0	1	1	0		$A\bar{B}\bar{C}$
	1	0	0	0		$\bar{A}+BC$
	1	0	1	1	$A\bar{B}C$	
	1	1	0	0		$\bar{A}\bar{B}C$
	1	1	1	0		$\bar{A}\bar{B}\bar{C}$

$$\# \Pi M = (A+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C}) (A+\bar{B}+\bar{C})$$

$$\Sigma_m = m_5, m_0, m_4$$

A	B	C	result	$\Sigma_m$	$\Pi M$
0	0	0	1	$\bar{A}\bar{B}\bar{C}$	
0	0	1	1	$\bar{A}\bar{B}C$	
0	1	0	0	<del><math>\bar{A}B\bar{C}</math></del>	$A\bar{B}C$
0	1	1	0	<del><math>\bar{A}B\bar{C}</math></del>	$A\bar{B}\bar{C}$
1	0	0	1	$A\bar{B}\bar{C}$	
1	0	1	1	$A\bar{B}C$	
1	1	0	1	$A\bar{B}\bar{C}$	
1	1	1	0	<del><math>\bar{A}B\bar{C}</math></del>	$\bar{A}\bar{B}\bar{C}$

$$\# \bar{x}\bar{z} + \bar{y}$$

$$SOP (\bar{x}y\bar{z}) + (\bar{x}\bar{y}\bar{z})$$

$\bar{x}$	$\bar{y}$	$\bar{z}$
0	0	0
0	1	0

$$(\bar{x}\bar{y}\bar{z}) + (x\bar{y}\bar{z}) + \\ (\bar{x}\bar{y}z) + (x\bar{y}z)$$

$\bar{x}$	$\bar{y}$	$\bar{z}$
0	0	0
1	0	0
0	0	1
1	0	1

$$\# \bar{x}y + y$$

$$SOP (\bar{x}y) + (xy) + (x\bar{y}) \\ + (\bar{x}\bar{y}) + (y) + (\bar{y})$$

$\bar{x}$	$y$
0	1
0	0
1	0
0	0

$$\# \Sigma(x, y, w, z)$$

$$(\bar{x}yz) + (xz) + (xw)$$

$$\bar{x}yzw$$

$$0110$$

$$0111$$

$$1110$$

$$1111$$

$$xyz^w$$

$$1010$$

$$1011$$

$$1100$$

$$1111$$

$$xyzw$$

$$1001$$


$$1011$$

$$1101$$

$$1111$$

$$(\bar{x}yz^w) + (\bar{x}yzw) + (x\bar{y}z^w) + (x\bar{y}zw) \\ + (xyz^w) + (xyzw) + (\bar{x}y^z w) + (\bar{x}y^z w) \\ - (\bar{x}\bar{y}zw) + (xy\bar{z}w) + (xyzw)$$
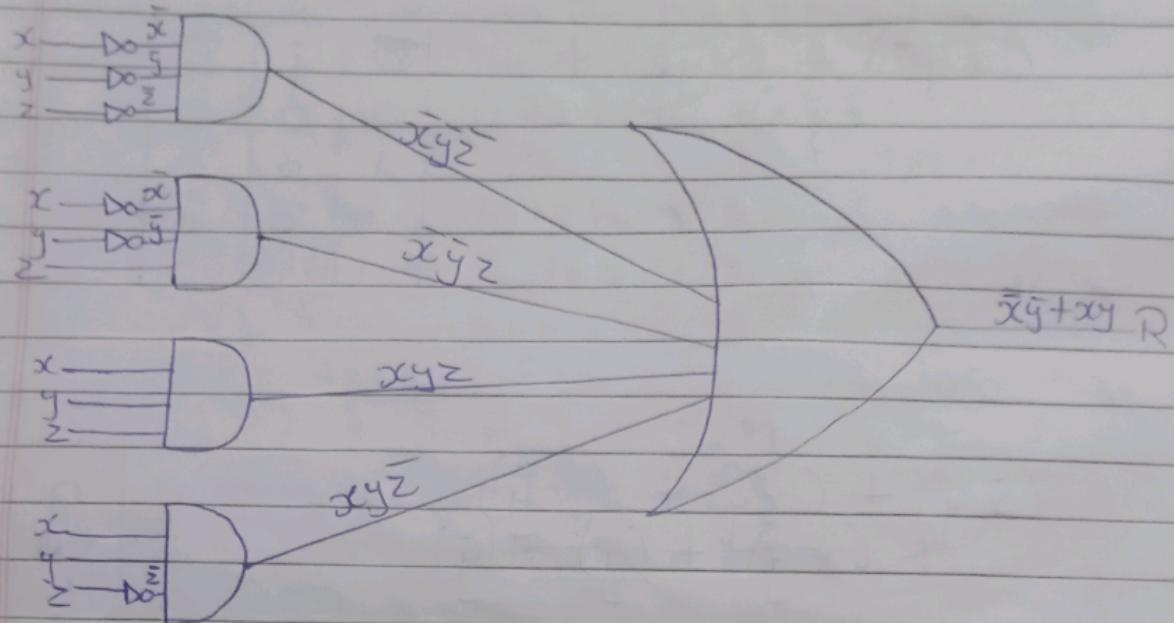
$$\begin{aligned} & \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + xy\bar{z} + xyz \\ & \bar{x}\bar{y}(\bar{z}+z) + xy(z+\bar{z}) \\ & \bar{x}\bar{y} + xy \end{aligned}$$



#

K - MAP

		$P$	$B$	0	1		$P$	$B$	00	01	11	10
$x$	$y$	0	00	01	→ Cell	0	000	001	011	010		
0	0	1	10	11		1	100	101	111	110		
0	1											
1	1											
		$A$	$C$	00	01	11	10					
1	0			00	0000 <sub>0</sub>	0001 <sub>1</sub>	0011 <sub>3</sub>	0010 <sub>2</sub>				
				01	0100 <sub>4</sub>	0101 <sub>5</sub>	0111 <sub>7</sub>	0110 <sub>6</sub>				
				11	1100 <sub>12</sub>	1101 <sub>13</sub>	1111 <sub>15</sub>	1110 <sub>14</sub>				
				10	1000 <sub>8</sub>	1001 <sub>9</sub>	1011 <sub>11</sub>	1010 <sub>10</sub>				

		$P$	$B$	0	1	
$A$	$B$	0	00	01		
1	10	11	13			

# ①  $\Sigma m(1, 3)$ 

$$\begin{aligned} & \bar{A}B + AB \\ & B(\bar{A} + A) \\ & = B \text{ Ans.} \end{aligned}$$

$$\textcircled{2} \quad \Sigma_m(A, B) = (0, 2)$$

A	B	0	1
0	00	01	
1	10	11	3

$$\begin{aligned}\bar{A}\bar{B} + A\bar{B} \\ \bar{B}(\bar{A}+A) \\ = \bar{B} \text{ Ans.}\end{aligned}$$

$$\textcircled{3} \quad \Sigma_m(A, B) = (0, 3)$$

A	B	0	1
0	00	01	
1	10	11	3

$$\bar{A}\bar{B} + AB$$

$$\textcircled{4} \quad \Sigma_m(A, B, C) = (0, 1, 4, 5)$$

A	B	C	00	01	11	10
0	0	0	000	001	011	010
1	1	0	100	101	111	110

$$\begin{aligned}\textcircled{1} \quad \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C \\ \bar{A}\bar{B}(\bar{C}+C)\end{aligned}$$

$$\begin{aligned}\textcircled{2} \quad \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\ A\bar{B}(\bar{C}+C)\end{aligned}$$

$$\textcircled{3} \quad (0, 4)$$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$\bar{B}\bar{C}(\bar{A}+A) = \bar{B}\bar{C} \text{ Ans.}$$

$$\textcircled{5} \quad \Sigma_m(A, B, C) = (0, 2, 5, 6, 7)$$

$$\begin{aligned}\textcircled{4} \quad (1, 5) \\ \bar{A}\bar{B} \text{ Ans.}\end{aligned}$$

$$\begin{aligned}\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\ \bar{B}\bar{C}(\bar{A}\bar{B} + A)\end{aligned}$$

$$\bar{B}\bar{C} - \text{Ans.}$$

A	B	C	00	01	11	10
0	0	0	000	001	011	010
1	1	0	100	101	111	110

$$\textcircled{1} \quad (0, 2)$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$\bar{A}\bar{C}(\bar{B}+B)$$

$$\bar{A}\bar{C} - \text{Ans.}$$

$$\textcircled{2} \quad (5, 7)$$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$AC(\bar{B}+B)$$

$$AC - \text{Ans.}$$

$$\textcircled{3} \quad (7, 6)$$

$$ABC + A\bar{B}\bar{C}$$

$$AB(C+\bar{C})$$

$$AB - \text{Ans.}$$

$$\textcircled{4} \quad (2, 6)$$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$\bar{C}B(\bar{A}+A)$$

$$\bar{C}B - \text{Ans.}$$

$$\textcircled{1} \quad \Sigma_m(A, B, C) = (0, 1, 2, 4)$$

A	BC	00	01	11	10
0	000	001	011	010	
1	100	101	111	110	

$$\textcircled{1} \quad (0, 1)$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$\bar{A}\bar{B} (\bar{C} + C)$$

$$\bar{A}\bar{B} - \text{Ans}$$

$$\textcircled{2} \quad (0, 2)$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$\bar{A}\bar{C} (\bar{B} + B)$$

$$\bar{A}\bar{C} - \text{Ans}$$

$$\textcircled{3} \quad (0, 4)$$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$\bar{B}\bar{C} (\bar{A} + A)$$

$$\bar{B}\bar{C} - \text{Ans}$$

$$\textcircled{2} \quad \Sigma_m (0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$$

$2^4(16)$

Pairing of  
BC

Pairing of  
D-Dms

$\checkmark D + \bar{B}\bar{C}$

Ans.

PB	CD	00	01	11	10
00	0000	0001	0011	0010	
01	0100	0101	0111	0110	
11	1100	1101	1111	1110	
10	1000	1001	1011	1010	

Pairing of 2  $\textcircled{1} \quad (0, 1)$

$$\bar{A}\bar{B}\bar{C}$$

$$\bar{A}\bar{B}CD$$

$$(8, 9)$$

$$(13, 15)$$

$$ABD$$

$$\textcircled{5} \quad (11, 15)$$

$$ACD$$

$$\textcircled{6} \quad (9, 11)$$

$$\bar{A}\bar{B}D$$

$$\textcircled{7} \quad (9, 13)$$

$$AC\bar{D}$$

$$\textcircled{8} \quad \Sigma_m (0, 1, 3, 5, 7, 8)$$

PB	CD	00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$\bar{A}D + \bar{B}\bar{C}\bar{D}$$

⑨  $f(u, x, y, z) = \text{sum}(1, 3, 4, 6, 9, 11, 12, 14)$

wz		00	01	11	10
00	0	1	3	1	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$\bar{w}\bar{z}z + w\bar{z}z + \bar{w}x\bar{z} + wx\bar{z}$$

$$\bar{x}z + x\bar{z}$$

⑩  $f(A, B, G, H) = \text{sum}(3, 4, 5, 7, 9, 13, 14, 15)$

AB		GH			
		00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

$$(3, 4, 5, 7, 13, 15), (4, 5), (13, 9), (14, 15), (13, 9)$$

$$BH + \bar{A}B\bar{G} + A\bar{G}H + ABG + \bar{A}GH$$

⑪  $f(x, u, v) = (1, 6, 4)$

x\uv	00	01	11	10	
0	0	1	3	2	(4, 6), (1)
1	4	5	7	6	$\bar{x}v + \bar{x}\bar{v}v$

⑫  $f(x, u, v) = (1, 3, 4)$

$$(1, 3), (4)$$

$$\bar{x}v + x\bar{v}v$$

$$\textcircled{13} \quad f(x, u, v) = (1, 2, 4)$$

$x \backslash u$	00	01	11	10
0	0	11	3	21
1	41	5	7	6

$$(1), (2), (4) \\ \bar{x}\bar{u}v + \bar{x}uv\bar{v} + \bar{x}v\bar{u}\bar{v}$$

$$\textcircled{14} \quad f(A, B, C) = (0, 1, 4, 5, 7, 6)$$

$A \backslash BC$	00	01	11	10
0	0	1	3	2
1	41	51	71	61

$$\Rightarrow (0, 1) \\ \bar{A}\bar{B} + A (4, 5, 7, 6)$$

$$\Rightarrow (0, 1, 4, 5) \\ \bar{B} + AB (7, 6)$$

$$\Rightarrow (4, 5, 7, 6) \\ A + \bar{B} (0, 1, 4, 5)$$

$$\textcircled{15} \quad \delta(A, B, C, D) = (0, 1, 2, 3, 4, 8, 9, 10, 11, 12)$$

$AB \backslash CD$	00	01	11	10	
00	0	1	3	2	$=(0, 1, 3, 2, 8, 9, 11, 10)$
01	4	5	7	6	$\bar{B}$
11	12	13	15	14	$(0, 4, 12, 8)$
10	8	9	11	10	$\bar{C}\bar{D}$

$$\textcircled{16} \quad (A, B, C, D) = (2, 5, 8, 10, 15)$$

		CD	00	01	11	10
		AB	00	01	11	10
AB	00	0				
	01	4		5	7	6
	11	12		13	15	14
	10	8	1	9	11	10

$$(8, 10), (2, 10), (5), (15)$$

$$\bar{A}\bar{B}\bar{D} + \bar{B}C\bar{D} + \bar{A}B\bar{C}D + ABCD$$

$$\textcircled{17} \quad (A, B, C, D) = (0, 2, 8, 10)$$

		CD	00	01	11	10
		AB	00	01	11	10
AB	00	0	1	3	2	1
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	1	9	11	10

$$(0, 2), (8, 10)$$

$$\bar{A}\bar{B}\bar{D} + A\bar{B}\bar{D}$$

$$\textcircled{18} \quad (A, B, C, D) = (1, 2, 4, 8, 10, 15)$$

		CD	00	01	11	10
		AB	00	01	11	10
AB	00	0	1	3	2	1
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	1	9	11	10

$$(1), (4), (15), (10, 2)$$

$$\bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + A\bar{B}CD + \bar{B}C\bar{D} + (10, 8)$$

$$A\bar{B}\bar{D}$$

$$\textcircled{19} \quad (A, B, C, D) = (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

		CD	00	01	11	10
		AB	00	01	11	10
AB	00	0	1	3	2	1
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	1	9	11	10

$$(0, 4, 12, 2, 6)$$

$$(0, 1, 4, 5, 12, 13, 8, 9), (2, 14)$$

$$\bar{C} + \bar{E} \oplus \bar{A}B\bar{C}X$$

$$\bar{B}CD$$

$$(0, 2)$$

$$+ \bar{A}\bar{B}\bar{D}$$

$$m, \Sigma = \text{SOP}$$

$$m, \Pi = \text{POS}$$

$$\underline{\underline{=}} xy'z + x'y'z + w'xy + wx'y + wxy$$

$$\text{Sol. } wxy'z$$

$$0101 \rightarrow 5$$

$$1101 \rightarrow 13$$

$$wx'y'z$$

$$0001 \rightarrow 1$$

$$1001 \rightarrow 9$$

$$w'x^2y z$$

$$01Y0 \rightarrow 6$$

$$0111 \rightarrow 7$$

$$w'x^1y z$$

$$10Y0 \rightarrow 10$$

$$1011 \rightarrow 11$$

$$w \quad x \quad y \quad z$$

$$1 \quad 1 \quad 1 \quad 0 \rightarrow 14$$

$$1 \quad 1 \quad 1 \quad 1 \rightarrow 15$$

$$\underline{\underline{=}} f(A, B, C, D) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$$

Sol.

		CD		B		A	
		00	01	11	10		
AB	00	0 X	1 1	3 X	2 1		
	01	4	5 X	7 1	6 1		
11	12 X	13 1	15 1	14 1			
10	8 1	9 1	11 1	10 1			

$$(8, 0), (12, 13, 15, 14), (1, 5, 3, 7), (3, 7, 2, 6)$$

$$\bar{B}\bar{C}\bar{D} * + AB * + \bar{A}D * + \bar{A}C$$

22 K-MAP

$$(5, 13, 1, 9, 6, 7, 10, 11, 14, 15)$$

		CD		B		A	
		00	01	11	10		
AB	00	0	1 1	3	2		
	01	4	5 1	7 1	6 1		
11	12	13 1	15 1	14 1			
10	8	9 1	11 1	10 1			

(1, 5, 13, 9), (7, 15, 6, 14), (11, 10)  
~~g x \* + g y \* + w y~~

pos

$$\underline{\underline{21}} \quad \prod (0, 5, 4, 6) = F(A, B, C)$$

A	BC	00	01	11	10
0	0 <sub>0</sub>	1 <sub>0</sub>	3 <sub>0</sub>	2 <sub>0</sub>	
1	4 <sub>0</sub>	5 <sub>0</sub>	7 <sub>0</sub>	6 <sub>0</sub>	

51

$$(BC)^* * (\bar{A}C) * (\bar{A} + B)$$

$$\underline{\underline{22}} \quad F(A, B, C, D) = \prod M(3, 4, 5, 7, 9, 13, 14, 15)$$

AB	CD	00	01	11	10
00	0	1	3 <sub>0</sub>	2 <sub>0</sub>	
01	4 <sub>0</sub>	5 <sub>0</sub>	7 <sub>0</sub>	6 <sub>0</sub>	
10	12 <sub>0</sub>	13 <sub>0</sub>	15 <sub>0</sub>	14 <sub>0</sub>	
11	8 <sub>0</sub>	9 <sub>0</sub>	11 <sub>0</sub>	10 <sub>0</sub>	

$$3, 7 + 4, 5 + 13, 9 + 15, 14 \\ (A\bar{C}\bar{D}) * (A + \bar{B} + C) * (\bar{A}\bar{B}\bar{D}) \\ * (\bar{A} + \bar{B} + \bar{C})$$

$$\underline{\underline{23}} \quad F(A, B, C, D) = M(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$$

AB	CD	00	01	11	10
00	0x	1 <sub>0</sub>	3x	2 <sub>0</sub>	
01	4	5x	7 <sub>0</sub>	6 <sub>0</sub>	
11	12x	13 <sub>0</sub>	15 <sub>0</sub>	14 <sub>0</sub>	
10	8 <sub>0</sub>	9 <sub>0</sub>	11 <sub>0</sub>	10 <sub>0</sub>	

$$(0, 1, 3, 2), (12, 13, 15, 14)^+ \\ (A + B) * (\bar{A} + \bar{B}) * (\bar{A} + \bar{C}) \\ * (\bar{A} + C + D)$$

$$\underline{\underline{24}} \quad F(W, X, Y, Z) = \prod M(5, 13, 1, 9, 6, 7, 10, 11, 14, 15)$$

WT	Z	00	01	11	10
00	0	1 <sub>0</sub>	3	2	
01	4	5 <sub>0</sub>	7 <sub>0</sub>	6 <sub>0</sub>	
11	12	13 <sub>0</sub>	15 <sub>0</sub>	14 <sub>0</sub>	
10	8	9 <sub>0</sub>	11 <sub>0</sub>	10 <sub>0</sub>	

$$(\bar{Y}\bar{Z}) * (\bar{X} + \bar{Y}) * (\bar{W} + \bar{Y})$$

$$\underline{\underline{25}} \quad (AB, C, D) = \Pi(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

$\bar{A}B$	$\bar{C}D$	00	01	11	10
00	00	0	10	3	20
01	40	50	7	60	
11	120	130	15	140	
10	80	90	11	100	

$$C * (\bar{A} + \bar{C} + D) * (\bar{B} + \bar{C} + D)$$

$$\underline{\underline{26}} \quad (A, B, C, D) = \Pi(1, 2, 4, 8, 10, 15)$$

$\bar{A}B$	$\bar{C}D$	00	01	11	10
00	0	0	10	3	20
01	40	5	7	6	
11	12	13	150	14	
10	80	9	11	100	

$$(A+B+C+\bar{D}) * (A+\bar{B}+C+D) * (\bar{A}+\bar{B}+\bar{C}+D)$$

$$* (B+\bar{C}+D) * (\bar{A}+B+D)$$

$$\underline{\underline{27}} \quad (AB, C, D) = \Pi(0, 1, 2, 3, 4, 8, 9, 10, 11, 12)$$

$\bar{A}B$	$\bar{C}D$	00	01	11	10
00	0	0	10	30	20
01	40	5	78	6	
11	120	13	15	14	
10	80	90	110	100	

$$(B) * (C+D)$$

$$\underline{\underline{28}} \quad F(W, X, Y, Z) = \Pi(1, 3, 4, 6, 9, 11, 12, 14)$$

$\bar{W}X$	$\bar{Y}Z$	00	01	11	10
00	0	0	10	30	2
01	40	5	7	60	
11	120	13	15	140	
10	8	90	110	10	

$$(x+z) * (\bar{x}+z)$$


$$\underline{\underline{29}} \quad F(AB, C, D) = \Pi(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$$

$\bar{A}B$	$\bar{C}D$	00	01	11	10
00	0	0	10	30	2
01	4	50	70	6	
11	12	130	150	14	
10	80	90	110	10	

$$(\bar{D}) * (B+C+D)$$
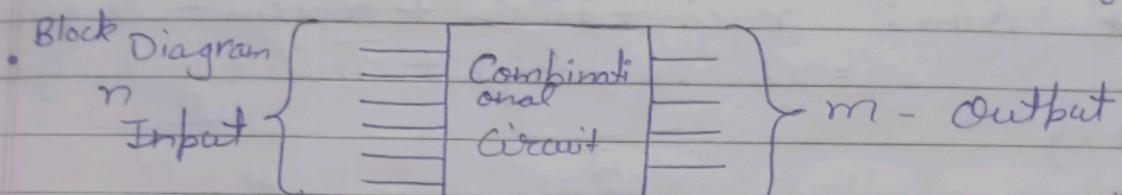
## # Combinational Circuits

- The output of Combinational circuit depends on the present state input.
- Input comes from external source and output goes to external destination.
- It has no memory.



### ★ Types of Combinational circuit :-

2-Input, 2-Output

#### 1) Half-adder

$$xy + \bar{y}z$$


logic function

		Sum	
x	y	0	1
0		0	1
1		2	3

$$\bar{x}y + x\bar{y}$$

EX-OR GATE

	x	y	Carry	Sum
0	0	0	0	0
1	0	1	0	1
2	1	0	0	1
3	1	1	1	0

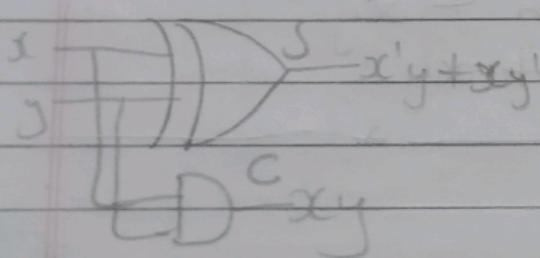

#### 2) Full-adder

$$\text{Sum} = \bar{x}\bar{y}\bar{c}_{in} + \bar{x}\bar{y}c_{in} + x\bar{y}\bar{c}_{in} + x\bar{y}c_{in}$$

	0	0	1	1	3*	2*	1
0	0	0	1	1	3*	2*	1
1	0	0	0	1	1	0	0
2	0	0	1	0	0	1	0
3	0	0	1	0	0	0	1
4	1	0	0	0	1	0	0
5	1	0	1	0	0	0	1
6	1	1	0	0	0	0	0
7	1	1	1	1	1	1	1

	x	y	c <sub>in</sub>	Sum	c <sub>out</sub>
0	0	0	0	0	0
1	0	0	1	1	0
2	0	0	0	0	0
3	0	0	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	0
7	1	1	1	1	1

$$\text{Carry} = x\bar{y}c_{in} + \bar{y}c_{in} + x\bar{y} + \bar{y}x = (x \oplus y)c_{in} + xy$$

★  $\bar{A}B + A\bar{B} = ?$

$$\begin{aligned}
 (\cancel{\bar{A}} + \bar{B}) (\cancel{\bar{A}} + \cancel{\bar{B}}) &= (A + \bar{B}) \cdot (\bar{A} + B) \\
 &= (A\bar{A} + AB + \bar{B}\bar{A} + \bar{B}B) \\
 &= 0 + AB + \bar{B}\bar{A} + 0 \\
 &= AB + \bar{B}\bar{A} \\
 &\equiv \text{EX-NOR} \\
 &\equiv A \odot B
 \end{aligned}$$

★ Sum:  $xyc_{in} + \bar{x}\bar{y}c_{in} + \bar{x}y\bar{c}_{in} + x\bar{y}\bar{c}_{in}$   
 $= c_{in}(x\bar{y} + \bar{x}\bar{y}) + \bar{c}_{in}(\bar{x}y + x\bar{y})$

$$\bar{w} = \bar{x}\bar{y} + xy$$

$$= X - \text{NOR}$$

$$w = \bar{x}y + x\bar{y}$$

$$= x \oplus y$$

$$= X - \text{OR}$$


$$\begin{aligned}
 &= c_{in}(\bar{w}) + \bar{c}_{in}(w) \\
 &\equiv \text{Cin } \oplus w \\
 &\equiv \text{Cin } \oplus x \oplus y
 \end{aligned}$$

[Sum Carry] Diagram :- 1st AND Gate then all AND GATE in OR GATE.

★ Carry:  $x c_{in} + y c_{in} + xy$   
 $= c_{in}(x + y) + xy$

— \* — \* — \* — \*




\* MULTIPLEXER is an electronic switch.

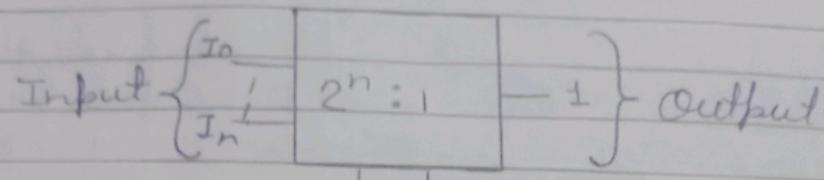

Select lines  $n$

$$\begin{array}{c} 2^n \\ \hline \begin{array}{|c|c|} \hline 2^1 = 2 & 2^3 = 8 \\ \hline 2^2 = 4 & 2^4 = 16 \\ \hline \end{array} \end{array}$$

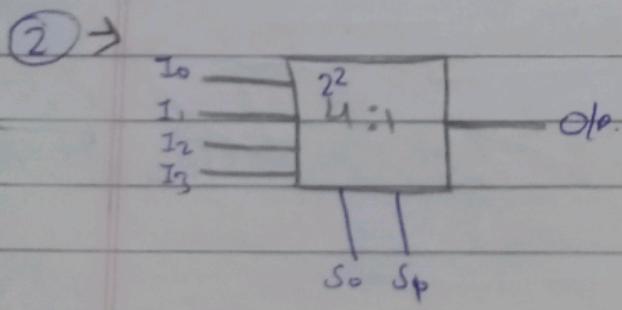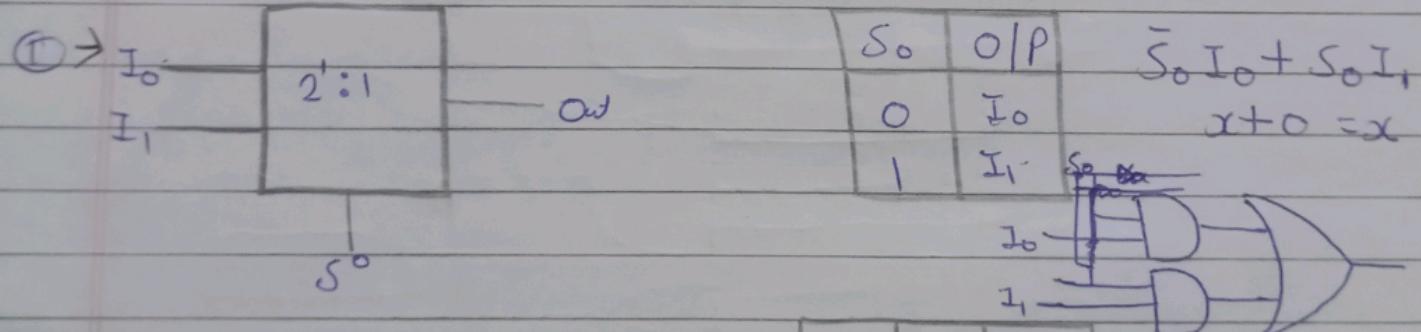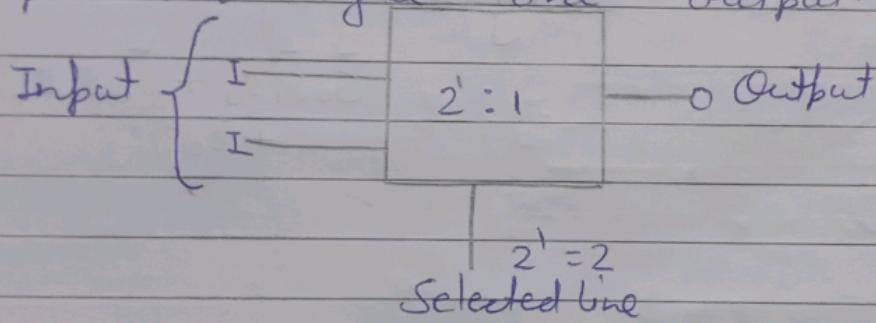
→ It is a combinational circuit which accept  $2^n$  inputs and give 1 output.  $n$  is the select line or control line. Accept Multiple Input and give one output.



$S_0$	$S_1$	O/P
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

$$\begin{aligned} \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_1 I_2 + S_0 S_1 I_3 \end{aligned}$$
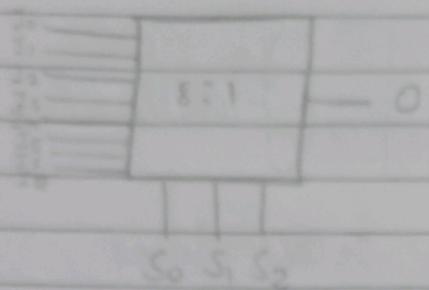
$$\textcircled{3} \rightarrow 2^3 = 8:1$$




$S_0$	$S_1$	$S_2$	O/P
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$\bar{I}_4$


$$\begin{aligned}
 & \bar{S}_0 \bar{S}_1 \bar{S}_2 I_0 + \bar{S}_0 \bar{S}_1 S_2 I_1 + \bar{S}_0 S_1 \bar{S}_2 I_2 \\
 & + \bar{S}_0 S_1 S_2 I_3 + S_0 \bar{S}_1 \bar{S}_2 I_4 + \\
 & S_0 \bar{S}_1 S_2 I_5 + S_0 S_1 \bar{S}_2 I_6 + S_0 S_1 S_2 I_7
 \end{aligned}$$

→ Circuit diagram of 4:1.
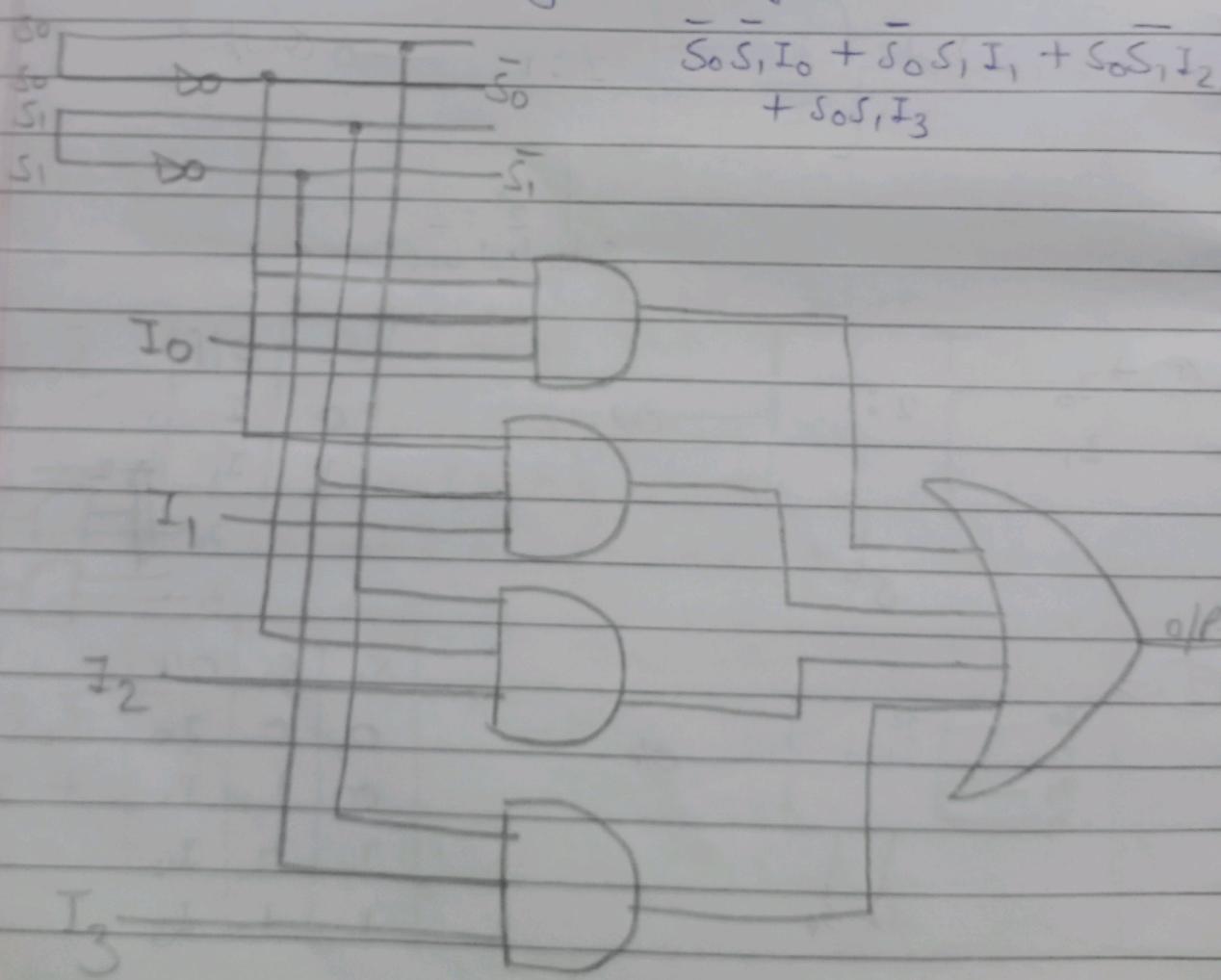
$$\begin{aligned}
 & \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_2 I_2 \\
 & + S_0 S_1 I_3
 \end{aligned}$$




$$\stackrel{4}{=} \Rightarrow 16:1$$

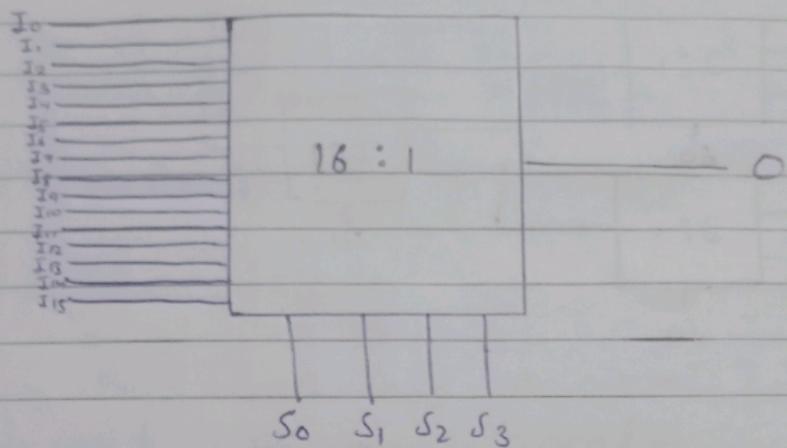


$S_0$	$S_1$	$S_2$	$S_3$	O/P
0	0	0	0	$I_0 \Rightarrow \bar{S}_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_0 + \bar{S}_0 \bar{S}_1 \bar{S}_2 S_3 I_1 +$
0	0	0	1	$\bar{S}_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_2 + \bar{S}_0 \bar{S}_1 S_2 S_3 + I_3 +$
0	0	1	0	$\bar{S}_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_4 + \bar{S}_0 \bar{S}_1 \bar{S}_2 S_3 I_5 +$
0	0	1	1	$\bar{S}_0 \bar{S}_1 S_2 \bar{S}_3 I_6 + \bar{S}_0 \bar{S}_1 S_2 S_3 I_7 +$
0	1	0	0	$S_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_8 + S_0 \bar{S}_1 \bar{S}_2 S_3 I_9 +$
0	1	0	1	$S_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_{10} + S_0 \bar{S}_1 \bar{S}_2 S_3 I_{11} +$
0	1	1	0	$S_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I_{12} + S_0 \bar{S}_1 \bar{S}_2 S_3 I_{13} +$
0	1	1	1	$S_0 \bar{S}_1 S_2 \bar{S}_3 I_{14} + S_0 \bar{S}_1 S_2 S_3 I_{15}$
1	0	0	0	$I_8$
1	0	0	1	$I_9$
1	0	1	0	$I_{10}$
1	0	1	1	$I_{11}$
1	1	0	0	$I_{12}$
1	1	0	1	$I_{13}$
1	1	1	0	$I_{14}$
1	1	1	1	$I_{15}$


5. 4:1

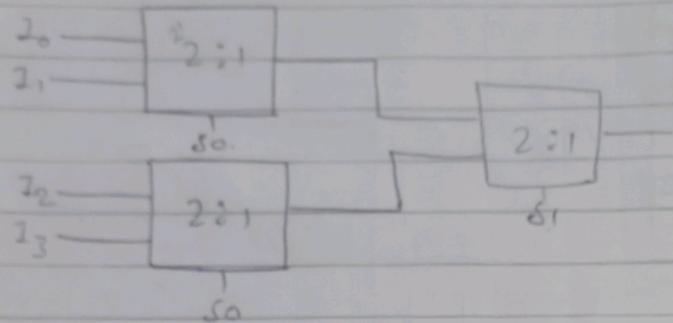


6. 8 : 1

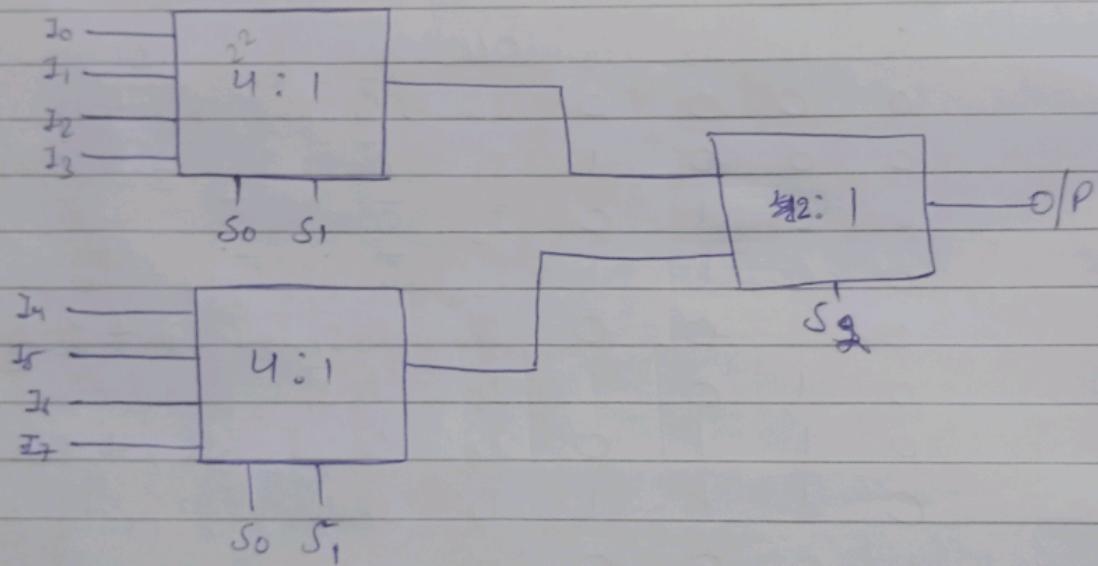


7. 16 : 1

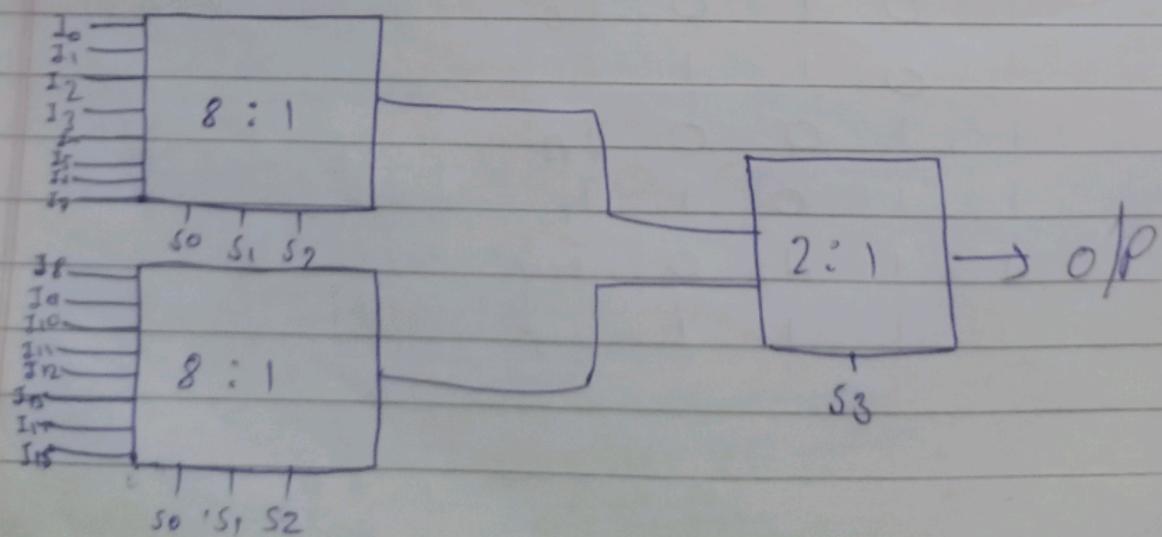

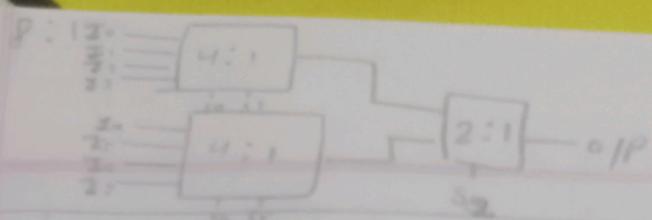


\* Demux :-

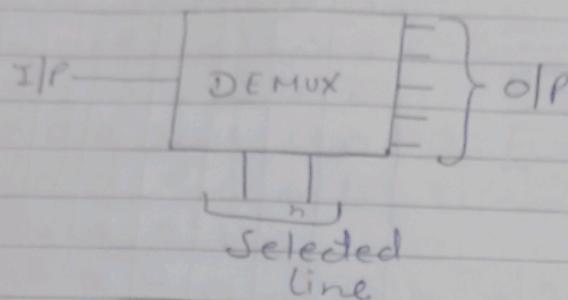


Demultiplexer is a combinational circuit which accepts a single input and gives multiple output or it can forward a single input to multiple output. For e.g.: 1 person has a file in a soft form. It can be the input for a printer or a fax machine that depends on the purpose of a file.


$\Rightarrow$

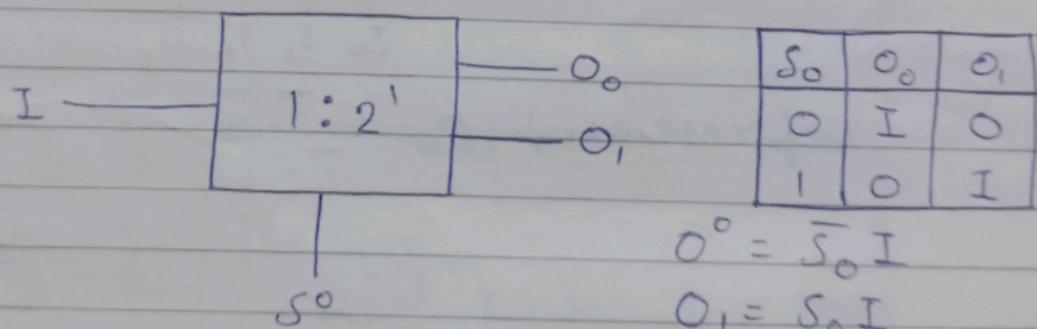

$\Rightarrow$

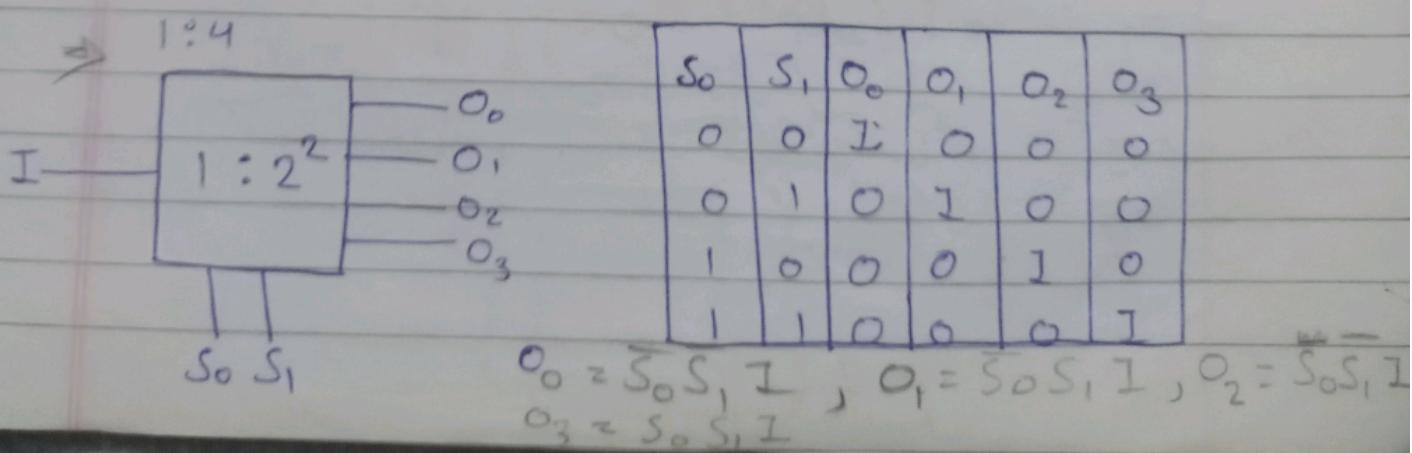

$\rightarrow 1:8$

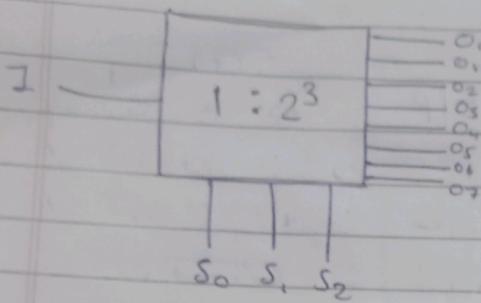


S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	O <sub>0</sub>	O <sub>1</sub>	O <sub>2</sub>	O <sub>3</sub>	O <sub>4</sub>	O <sub>5</sub>	O <sub>6</sub>	O <sub>7</sub>
0	0	0	I	0	0	0	0	0	0	0
0	0	1	0	I	0	0	0	0	0	0
0	1	0	0	0	I	0	0	0	0	0
0	1	1	0	0	0	I	0	0	0	0
1	0	0	0	0	0	0	I	0	0	0
1	0	1	0	0	0	0	0	I	0	0
1	1	0	0	0	0	0	0	0	I	0
1	1	1	0	0	0	0	0	0	0	I

$$O_0 = \bar{S}_0 \bar{S}_1 \bar{S}_2 I, \quad O_1 = \bar{S}_0 \bar{S}_1 S_2 I, \quad O_2 = \bar{S}_0 S_1 \bar{S}_2 I,$$

$$O_3 = \bar{S}_0 S_1 S_2 I, \quad O_4 = S_0 \bar{S}_1 \bar{S}_2 I, \quad O_5 = S_0 \bar{S}_1 S_2 I,$$

$$O_6 = S_0 S_1 \bar{S}_2 I, \quad O_7 = S_0 S_1 S_2 I$$

$\Rightarrow 1:16$

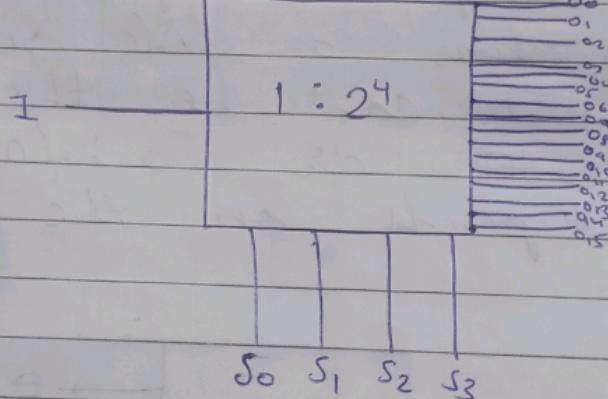

expression :-

$$O_0 = \bar{S}_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I, \quad O_1 = \bar{S}_0 \bar{S}_1 \bar{S}_2 S_3 I,$$

$$O_2 = \bar{S}_0 \bar{S}_1 S_2 \bar{S}_3 I, \quad O_3 = \bar{S}_0 \bar{S}_1 S_2 S_3 I,$$

$$O_4 = \bar{S}_0 S_1 \bar{S}_2 \bar{S}_3 I, \quad O_5 = \bar{S}_0 S_1 \bar{S}_2 S_3 I, \quad O_6 = \bar{S}_0 S_1 S_2 \bar{S}_3 I,$$

$$O_7 = \bar{S}_0 S_1 S_2 S_3 I, \quad O_8 = S_0 \bar{S}_1 \bar{S}_2 \bar{S}_3 I,$$

$$O_9 = S_0 \bar{S}_1 \bar{S}_2 S_3 I, \quad O_{10} = S_0 \bar{S}_1 S_2 \bar{S}_3 I,$$

$$O_{11} = S_0 S_1 \bar{S}_2 \bar{S}_3 I, \quad O_{12} = S_0 S_1 \bar{S}_2 S_3 I,$$


$$O_{13} = S_0 S_1 S_2 \bar{S}_3 I, \quad O_{14} = S_0 S_1 S_2 S_3 I,$$

$$O_{15} = S_0 S_1 S_2 S_3 I$$

SE

0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0  
0 0 0 0 1 0 0 0 0 0 0 0 0 0 0 0  
0 0 0 1 0 1 0 0 0 0 0 0 0 0 0 0  
0 0 1 0 0 0 1 0 0 0 0 0 0 0 0 0  
0 0 1 1 0 0 0 1 0 0 0 0 0 0 0 0  
0 1 0 0 0 0 0 0 1 0 0 0 0 0 0 0  
0 1 0 1 0 0 0 0 0 1 0 0 0 0 0 0  
0 1 1 0 0 0 0 0 0 1 0 0 0 0 0 0  
0 1 1 1 0 0 0 0 0 0 1 0 0 0 0 0  
1 0 0 0 0 0 0 0 0 0 0 1 0 0 0 0  
1 0 0 1 0 0 0 0 0 0 0 1 0 0 0 0  
1 0 1 0 0 0 0 0 0 0 0 1 0 0 0 0  
1 0 1 1 0 0 0 0 0 0 0 0 1 0 0 0  
1 1 0 0 0 0 0 0 0 0 0 0 0 1 0 0  
1 1 0 1 0 0 0 0 0 0 0 0 0 0 1 0  
1 1 1 0 0 0 0 0 0 0 0 0 0 0 0 1  
1 1 1 1 0 0 0 0 0 0 0 0 0 0 0 0

⇒ Diagram 1:4

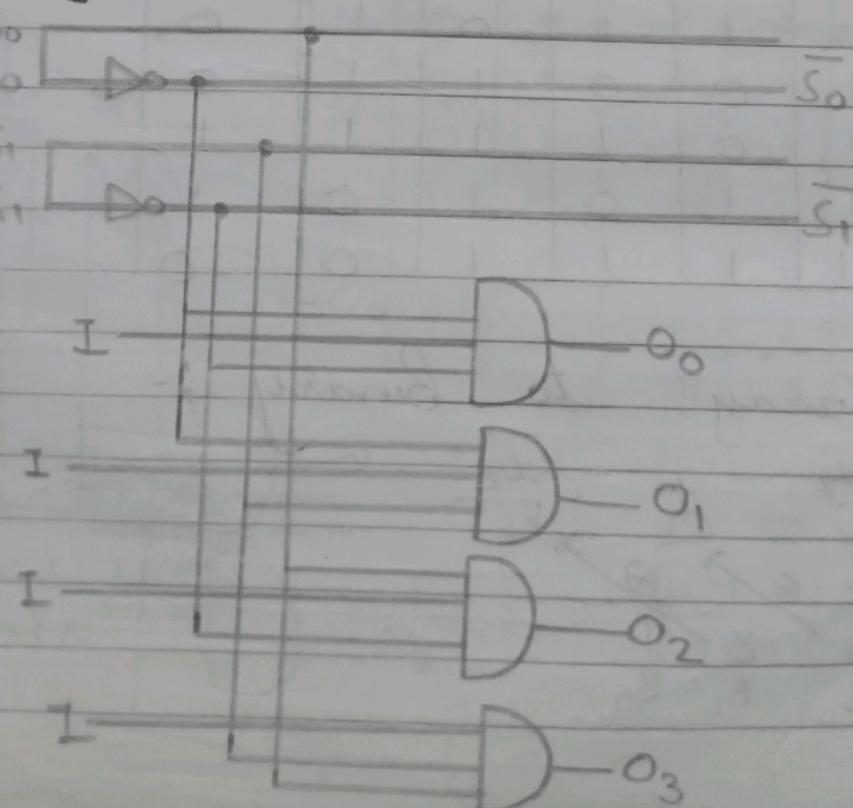

\* Binary to Gray code converter :-

A	B	$A \oplus B$	$x_3$	$x_2$	$x_1$	$x_0$
0	0	0	0	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	0	1	0	1	1

Most significant bit      Least sig. bit.

$\rightarrow$  Copy the MSB bit as it.


$\rightarrow$  To find out the next bit in the gray code you have to perform  $x_3 \oplus x_2$ . for the e.g given above

$$\Rightarrow 10001000010001 \rightarrow 11110111$$

$$\Rightarrow 01000010001 \rightarrow 01100011001$$

$B_2$	$B_1$	$B_0$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

\* Gray to Binary :-

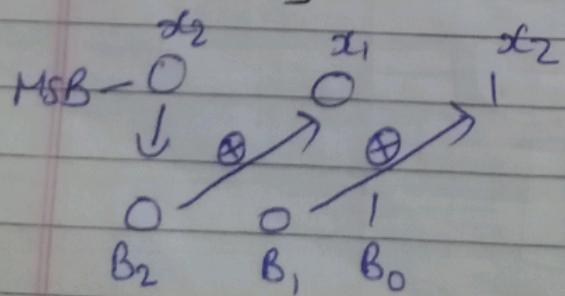

→ In gray to binary conversion, copy the MSB as given in the above e.g.

$$\Rightarrow 100100 \rightarrow 111000$$

⇒ 16 Bits.

B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	0	1
0	0	1	1	0	0	0	1
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	0
1	0	0	0	0	1	0	0
1	0	0	1	1	0	1	1
1	0	1	0	0	1	0	1
1	0	1	1	1	1	0	0
1	1	0	0	0	1	0	1
1	1	0	1	1	0	1	1
1	1	1	0	0	1	0	0
1	1	1	1	1	1	0	0


① G to B

10011101  
111010110

② B to G

101101001111  
100101010000


③ 8 : 1 Demux

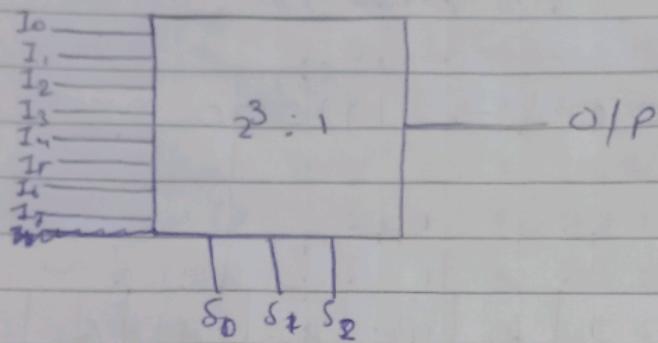

Truth Table

$S_0$	$S_1$	$S_2$	$O/P$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

Logic expression for O/P:
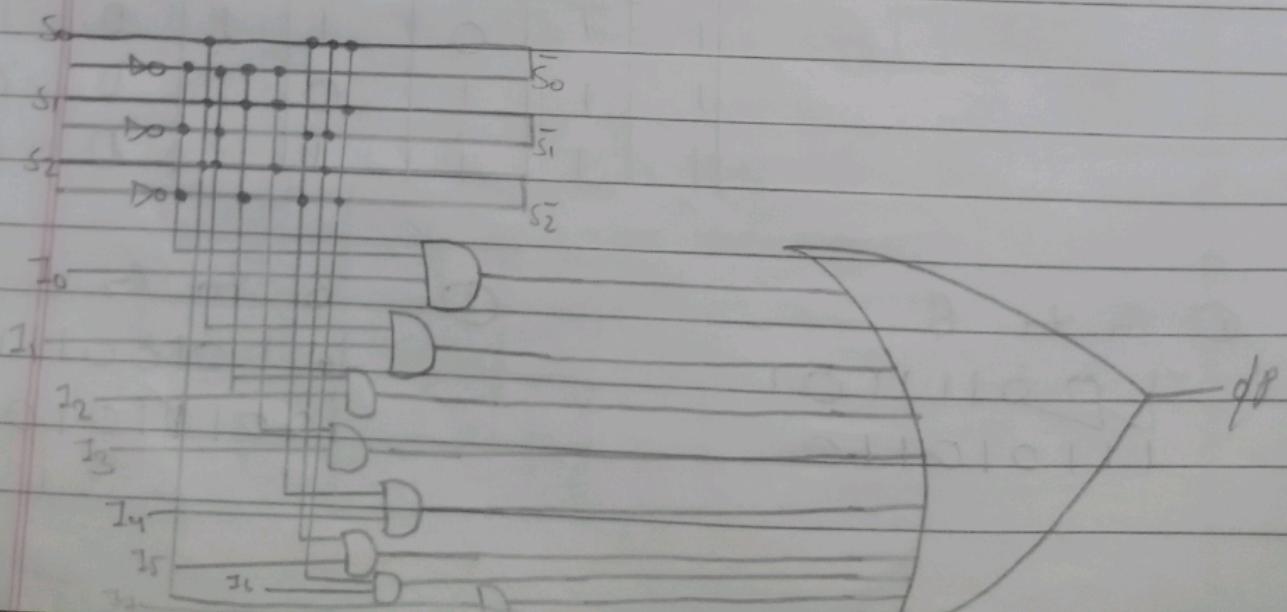
$$\bar{S}_0 \bar{S}_1 \bar{S}_2 I_0 + \bar{S}_0 \bar{S}_1 S_2 I_1 + \bar{S}_0 S_1 \bar{S}_2 I_2 + \bar{S}_0 S_1 S_2 I_3 + S_0 \bar{S}_1 \bar{S}_2 I_4 + S_0 \bar{S}_1 S_2 I_5 + S_0 S_1 \bar{S}_2 I_6 + S_0 S_1 S_2 I_7$$


encoder  $\Rightarrow$  2<sup>n</sup> I/P 3<sup>n</sup> O/P

decoder  $\Rightarrow$  n 2<sup>n</sup> SE  
I/P O/P

# encoder :-

2 <sub>0</sub>	2 <sub>1</sub>	2 <sub>2</sub>	2 <sub>3</sub>	2 <sub>4</sub>	2 <sub>5</sub>	2 <sub>6</sub>	2 <sub>7</sub>	0 <sub>0</sub>
0	0	0	0	0	0	0	1	0 <sub>1</sub>
0	0	0	0	0	0	0	1	0 <sub>2</sub>
0	0	0	0	0	0	1	0	1 <sub>0</sub>
0	0	0	0	0	1	0	0	1 <sub>1</sub>
0	0	0	0	1	0	0	0	1 <sub>2</sub>
0	0	0	1	0	0	0	0	1 <sub>3</sub>
0	1	0	0	0	0	0	0	1 <sub>4</sub>
1	0	0	0	0	0	0	1	1 <sub>5</sub>


I <sub>3</sub>	I <sub>6</sub>	I <sub>5</sub>	I <sub>7</sub>	I <sub>4</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	0	1	0	0	1
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	1	0	0	0	0	0	0	0	1	0
1	0	0	0	0	0	0	0	1	1	1

$$O_0 = I_1 + I_3 + I_5 + I_7$$

$$O_1 = I_2 + I_3 + I_6 + I_7$$

$$O_2 = I_4 + I_5 + I_6 + I_7$$

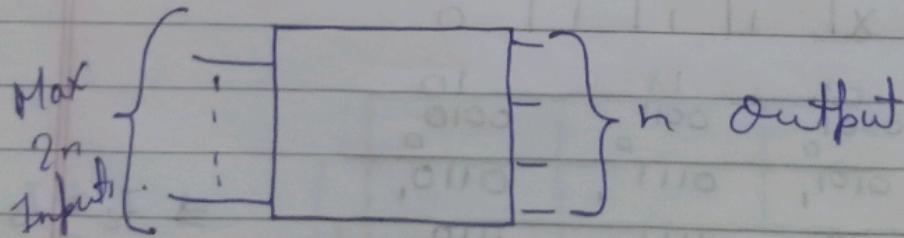Encoder is a combinational circuit which accepts max. 2<sup>n</sup> input & give n outputs. encoder converts the code into binary format. for e.g BCD to Binary encoder.



BCD (Binary Coder Decimal (0-9))

228  
Decoder

SE  
FOOD

$I_9$	$I_8$	$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
1	0	0	0	0	0	0	0	0	0	1	0	0	1

$$O_0 \rightarrow I_1 + I_3 + I_5 + I_7 + I_9$$

$$O_1 \rightarrow I_2 + I_3 + I_6 + I_7$$

$$O_2 \rightarrow I_4 + I_5 + I_6 + I_9$$

$$O_3 \rightarrow I_8 + I_9$$

(W-15)

Don't care

Parity :- It is

concept to detect errors  
A single bit error is

detected by it

### \* Priority encoder

$I_3$	$I_2$	$I_1$	$I_0$	$O_1$	$O_0$	V	Invalid
0	0	0	0	X	X	0	1
0	0	0	1	0	0	1	0
0	0	1	X	0	1	1	0
0	1	X	X	1	0	1	0
1	X	X	X	1	1	1	0

$O_1$

$I_3$	$I_2$	$I_1$	$I_0$	$O_1$	$O_0$	$I_1$	$I_0$
00	0000	X		00001	0	00110	0
01	0100,			0101,		0111,	0110,
11	1100,			1101,		1111,	1110,
10	1000,			1001,		1011,	1010,


$\Rightarrow I_2 + I_3$

SE

$I_3, I_2$	00	01	11	10
00	00	X	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010


$\Rightarrow I_3 + \bar{I}_2 I_1$

⇒ Decoder

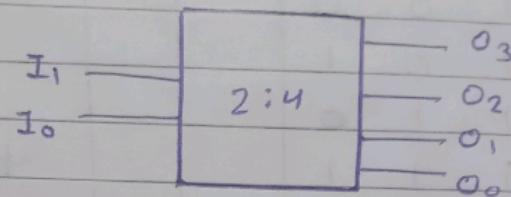

$I_1$	$I_0$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0
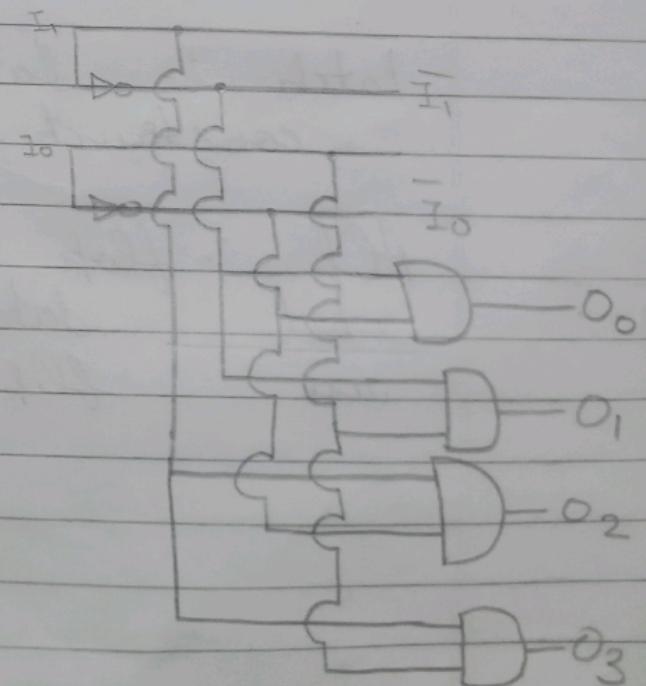
$$\begin{aligned}
 O_0 &\Rightarrow \bar{I}_1, \bar{I}_0 \\
 O_1 &\Rightarrow \bar{I}_1, I_0 \\
 O_2 &\Rightarrow I_1, \bar{I}_0 \\
 O_3 &\Rightarrow I_1, I_0
 \end{aligned}$$



## Binary to BCD

$I_3$	$I_2$	$I_1$	$I_0$	$O_9$	$O_8$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1										1
0	0	1	0										1
0	0	1	1										1
0	1	0	0										1
0	1	0	1										1
0	1	1	0										1
0	1	1	1										1
1	0	0	0	.	.	.	.	.	.	.	.	.	
1	0	0	1	.	.	.	.	.	.	.	.	.	

\* ~~Latch~~ :- In the sequential circuit output depend on current input and past output for e.g. latch, flip flop

Latch :- latch is used to construct the flip flop.


Flip - flop :- To store one bit data we have to use flip flop.

## NAND GATE


X	Y	R	$\bar{R}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

## SR Latch

S	R	$Q_{nt+1}$
0	0	invalid
0	1	1
1	0	0
1	1	HOLD

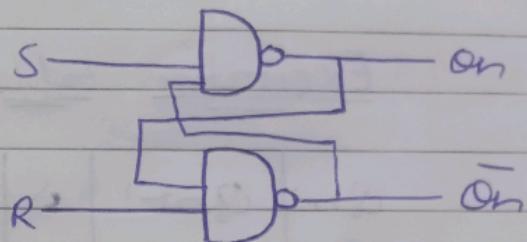

## SR flip-flop

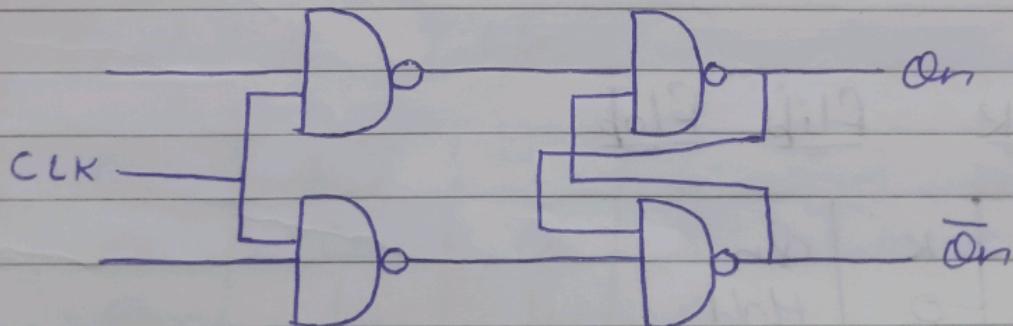

S	R	on
0	0	HOLD
0	1	0
1	0	1
1	1	INVALID HOLD

## Characteristic table


S	R	Qn	Qn+1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Invalid
1	1	1	Invalid

## Excitation table

Qn	Qn+1	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

## JK    flip-flop

J	K	Qn
0	0	Hold
0	1	0
1	0	1
1	1	Toggle

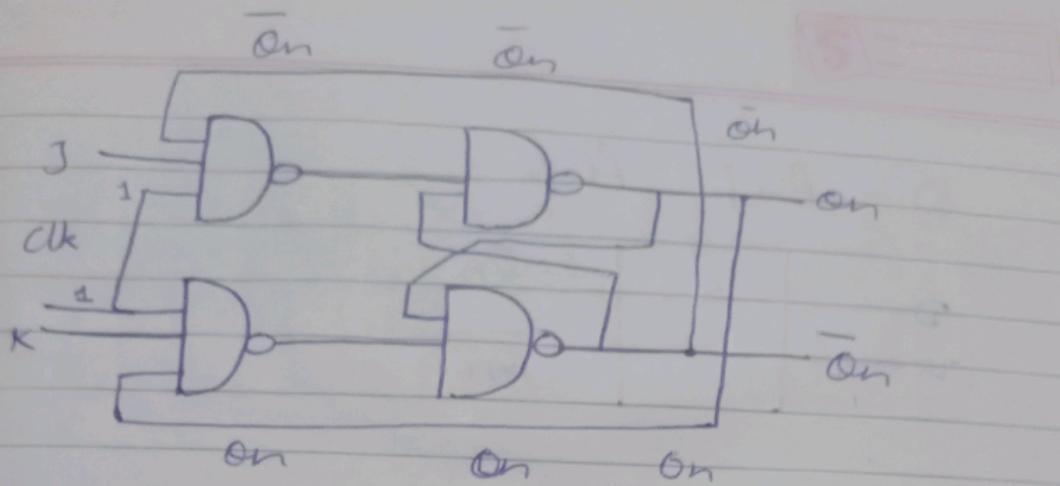

characteristic table

J	K	Qn	Qnt
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



Excitation Table

Qn	Qnt	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

	KA <sub>00</sub>	01	10	10
0	0	1	3	2
1	4	5	7	6

$$\Rightarrow \bar{K}Qn + J\bar{Q}n$$

## D - Flip flop

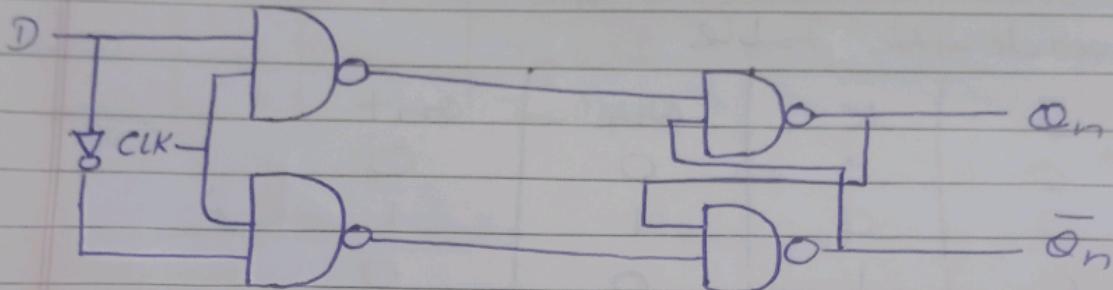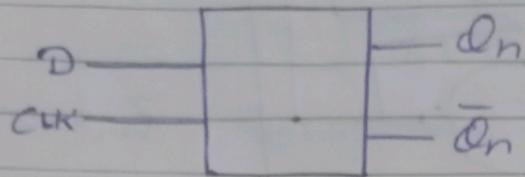

D	Qn
0	0
1	1

→ Truth table

## Characteristic table

D	Qn	Qn+1	D	Qn+1	1
0	0	0	0	0	1
0	1	0	1	2	1
1	0	1	1	X	1
1	1	1	X	X	1

## Excitation table

Qn+1	Qn	D
0	0	0
0	1	0
1	0	0
1	1	1

T - flip flop

T	$Q_{n+1}$
0	$\bar{Q}_n$
1	$\bar{Q} \bar{Q}_n$

Characteristics Table

T	$Q_n$	$Q_{n+1}$	<del>T-Q<sub>n+1</sub></del>
0	0	0	D
0	1	1	
1	0	1	
1	1	0	

T	$Q_n$	0	1
0	0	1	1
1	2	1	3


$$\bar{T}Q_n + T\bar{Q}_n$$

Excitation Table


$Q_{n+1}$	$Q_n$	T	<del><math>Q_n</math></del>	$Q_{n+1}$	$\bar{Q}_{n+1}$	$Q_{n+1} \oplus Q_n$
0	0	0	0	0	1	1
0	1	1	0	0	1	1
1	0	1	0	1	0	1
1	1	0	1	2	1	3

$$Q_{n+1} \oplus Q_n$$


\* Race Round Condition

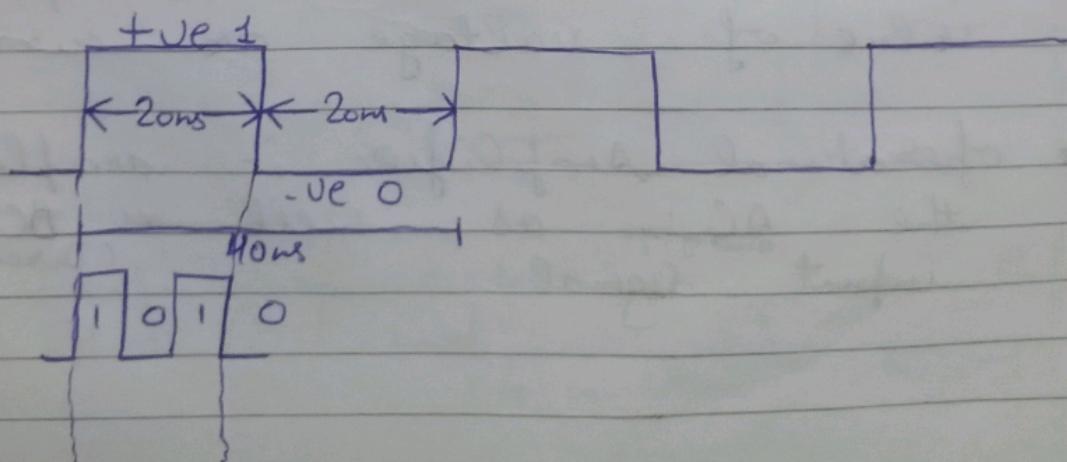

Master slave JK Flip Flop.

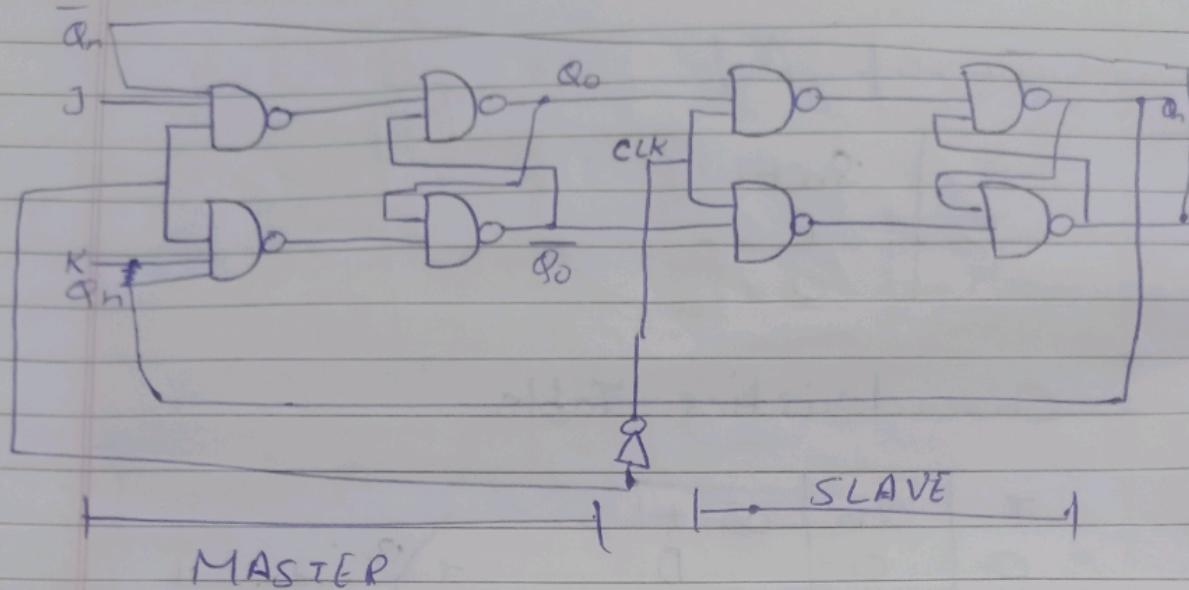


\* Digital to Analog converter (DAC)

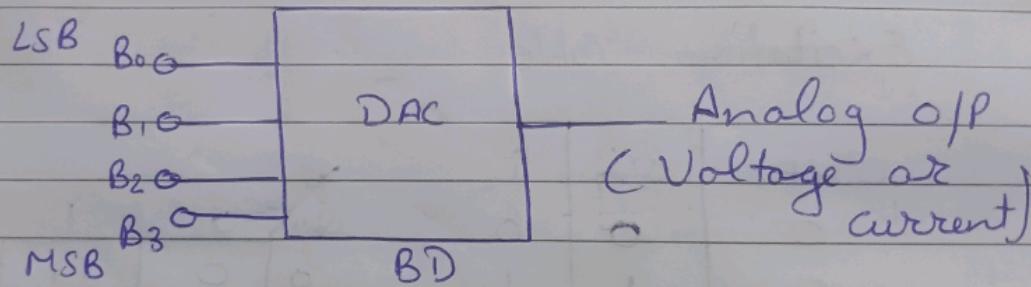

DAC :- It receives the I/P in the form of binary digits and convert it into corresponding value of voltage or current.

\* operational Amplifier :- amplifies the <sup>Analog!</sup> input signal as well as <sub>DC</sub> <sup>(Direct current)</sup> BC.

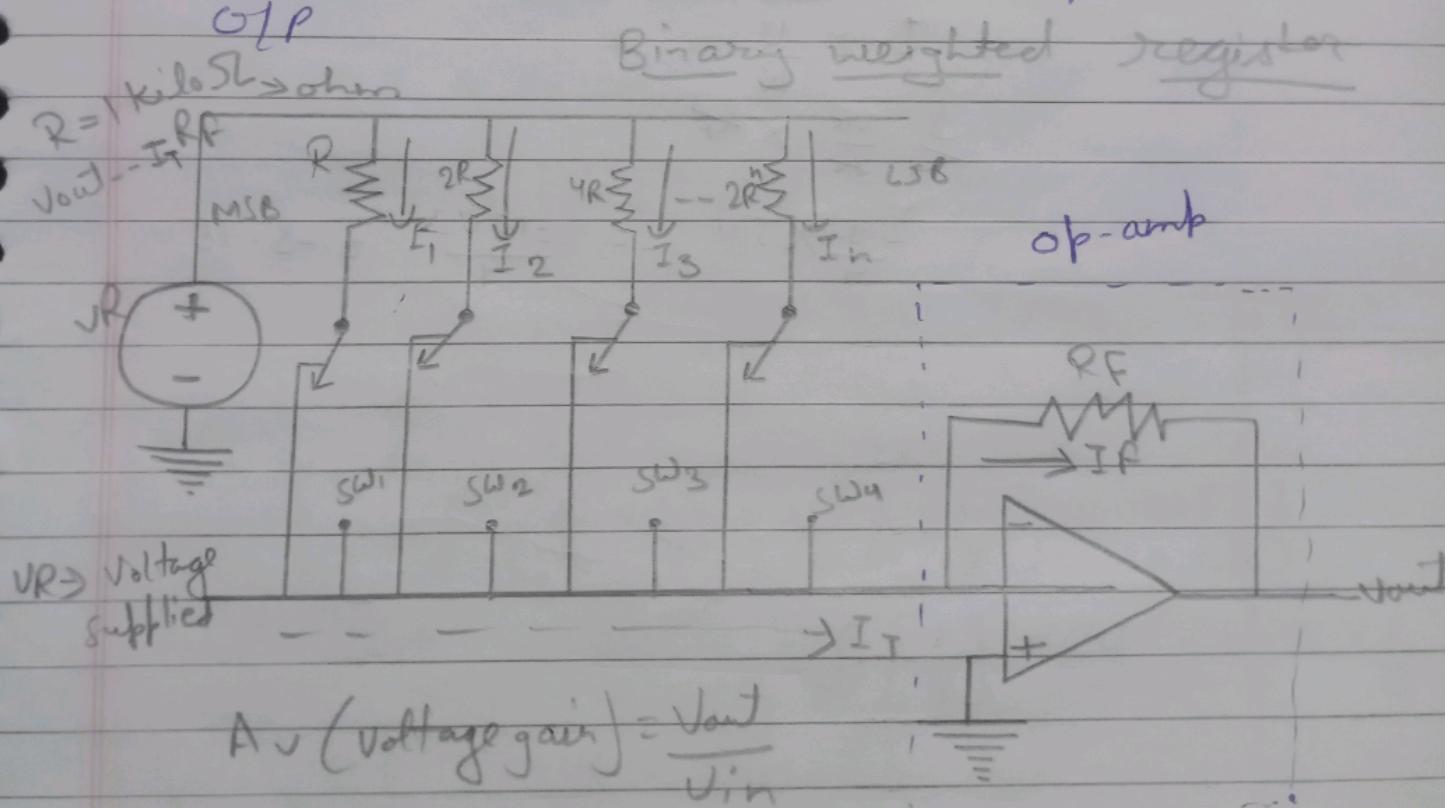- \* Resolution :- It is the smallest change occur due to change in input.
- \* Accuracy :- How much the actual o/p is matching with the expected o/p.
- \* Full scale range (FSR) :- Maximum o/p signal for the DAC.
- \* Settling time :- every digital signal take some time to produce the o/p



$I_T \rightarrow$  Total current

$R_f \rightarrow$  Feed back resistor

(to control the voltage gain)

$R_B$  &  $R_F = 1 \text{ Kilo ohm } \Omega$

SE

$$V_{out} = I_T R_F$$

$$\frac{V_{out}}{R_F}$$

MSB

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$I_T = \cancel{\frac{VR}{R}}^{\text{Voltage}} + \frac{VR}{2R} + \frac{VR}{4R} + \frac{VR}{8R}$$

$$\frac{VR}{R} \left[ \frac{1}{2} + \frac{1}{4} \right]$$

$$\frac{VR}{R} \left[ \frac{2+1}{4} \right] \frac{3}{4}$$


$$\frac{VR}{R} \times \frac{3}{4}$$

$$\therefore V = I_R \text{ total current}$$

$$I = \frac{V}{R}$$

$$\frac{3}{4} \frac{VR}{R} \times R_F$$
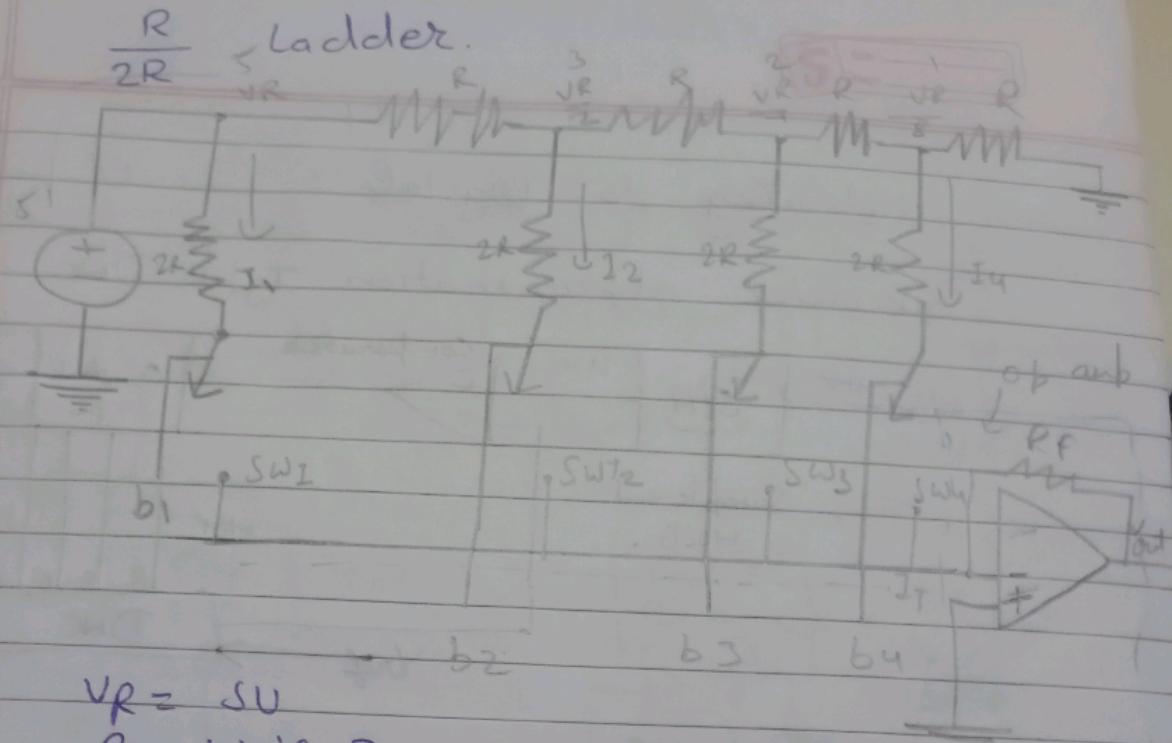
$$-\frac{3}{4} \times 5V = -\frac{15V}{4} = -3.75V$$



$$V_R = 5U$$

$$R = 1 \text{ Kilo } \Omega$$

$$R_F = 1 \text{ Kilo } \Omega$$

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$= V_R + \frac{V_R/2R}{2R} + \frac{VR/2R}{4R} + \frac{VR/2R}{8R}$$

$$= \frac{VR}{4R} + \frac{VR}{8R}$$

$$= \frac{VR}{R} \left[ \frac{1}{4} + \frac{1}{8} \right] = \frac{VR}{R} \left[ \frac{2+1}{8} \right] = \frac{VR}{R} \left[ \frac{3}{8} \right]$$


$$V_{out} = -I_F R_F = -\frac{VR}{R} \left[ \frac{3}{8} \right] \times R_F = -VR \times \frac{3}{8}$$

$$VR = 5U$$


$$= -5V \times \frac{3}{8} = -\frac{15U}{8}$$

Analog to Digital


Successive approximation type DAC.

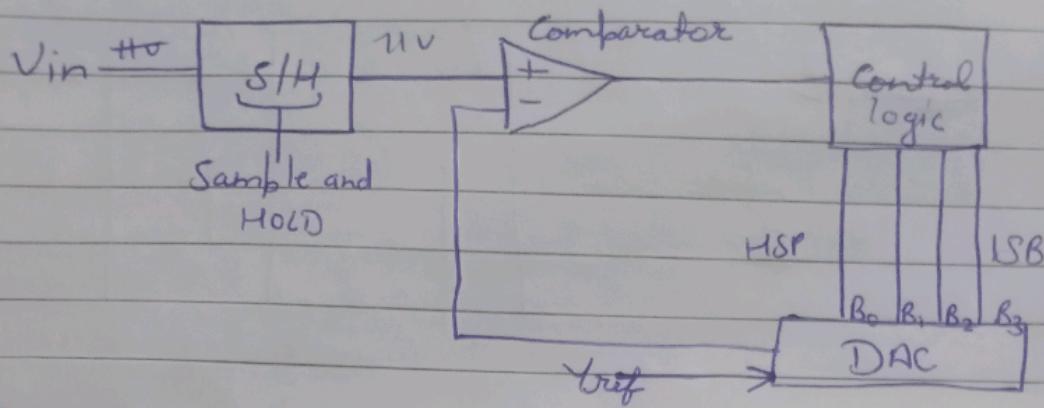

Control logic :-

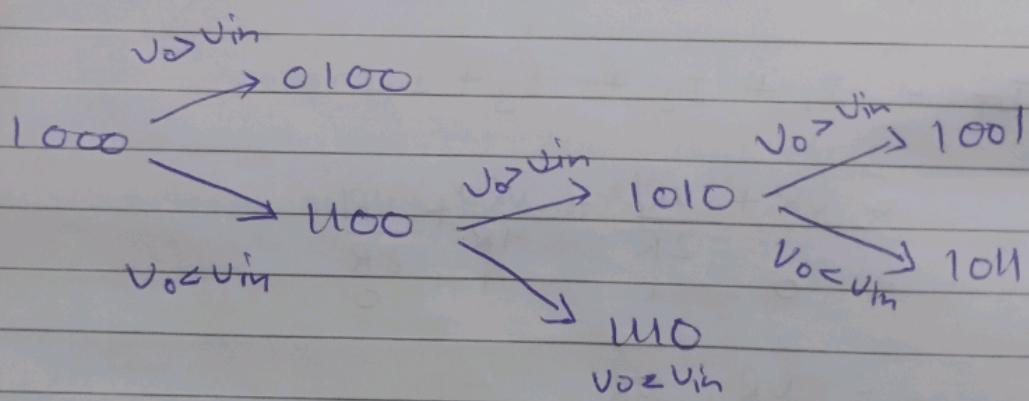

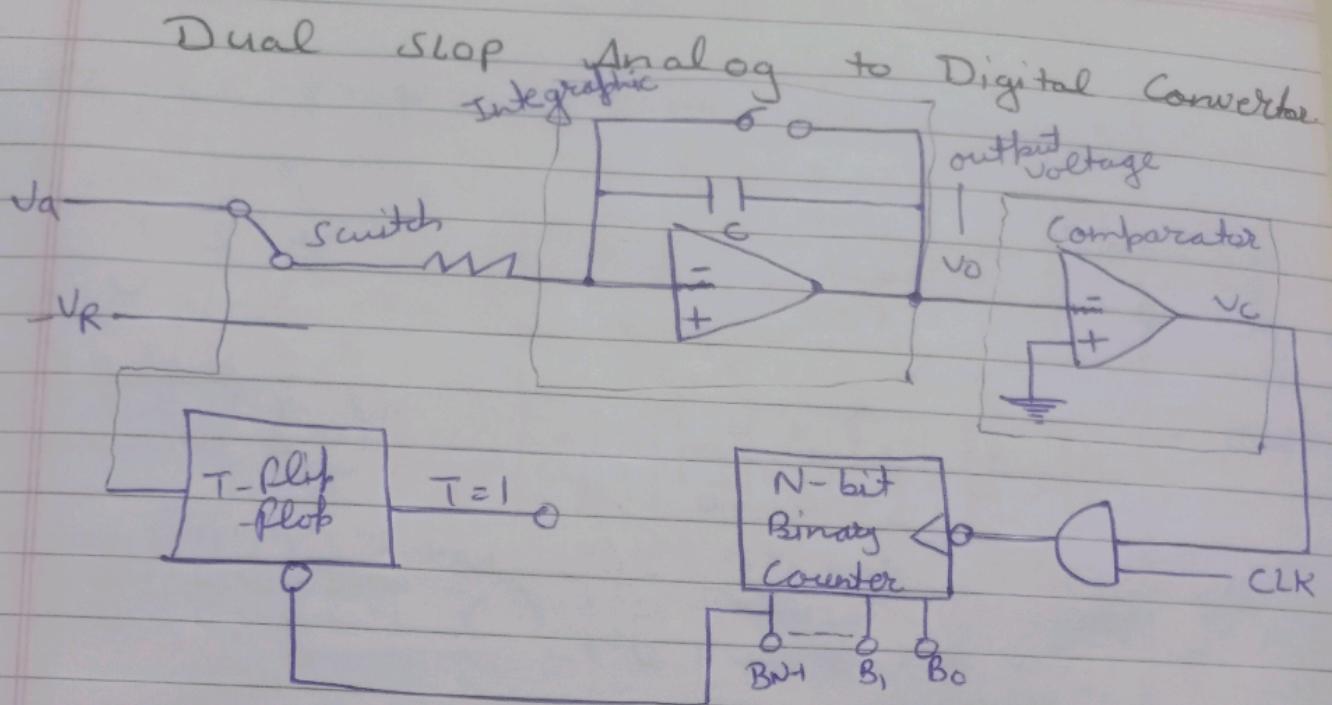Initial O/P for successive approx register is 1000.



$V_a$  = Analog voltage that we want to convert in Digital form.

$V_R$  = Reference voltage

$$V_o = \frac{1}{RC} \int_0^t V_a dt \approx \frac{1}{RC} V_a t$$